

Welcome to

DESIGNCON[®] 2023

WHERE THE CHIP MEETS THE BOARD

Conference

January 31 – February 2, 2023

Santa Clara Convention Center

Expo

February 1 – 2, 2023



VRM Modeling and Stability Analysis for the Power Integrity Engineer

Steve Sandler, Picotest.com

Benjamin Dannan, Northrop Grumman

Heidi Barnes, Keysight Technologies

*Steve Sandler (Picotest), Benjamin Dannan (Northrop Grumman),
Heidi Barnes (Keysight Technologies), Christian Yots (Texas Instruments)*



SPEAKERS



Steve Sandler

Managing Director, Picotest

Steve@Picotest.com | Picotest.com |
@stevenmsandler

Steve Sandler has been involved with power system engineering for more than 40 years. The founder and CEO of [Picotest.com](https://www.picotest.com), a company specializing in instruments and accessories for high-performance power system and distributed system testing



Heidi Barnes

Power Integrity Applications, Keysight Technologies

heidi_barnes@keysight.com | Keysight.com |

Senior Application Engineer in the PSS EDA Group of Keysight Technologies. Her recent activities include the application of electromagnetic, transient, and channel simulators to solve signal and power integrity challenges. Author of over 20 papers on SI and PI and recipient of the DesignCon 2017 Engineer of the Year.



Benjamin Dannan

Technical Fellow, Northrop Grumman

benjamin.Dannan@ngc.com | northropgrumman.com

Benjamin Dannan is a Technical Fellow and an experienced signal and power integrity (SI/PI) design engineer, advancing high-performance ASICs and high-speed digital designs. He is a Keysight ADS Certified Expert with numerous publications on SI/PI-related topics and received the prestigious DesignCon best paper award in 2020.



Outline

- **Why use a Sandler State-Space Average Model (SSAM)**
- **Populating the Sandler State-Space Model with design parameters and measurements**
- **Example: Building the TI TPS7H4003 SSAM**
- **The Digital Twin SSAM with PCB effects predicts measurement**
- **Results: TPS7H4003 SSAM vs. Simple L-R VRM SPICE model with and without PCB effects**
- **Call to action**
- **Summary**




Modeling a Switched Mode Power Supply



TI TPS7H4003 4-phase EVM

This model works for all forward VRM topologies

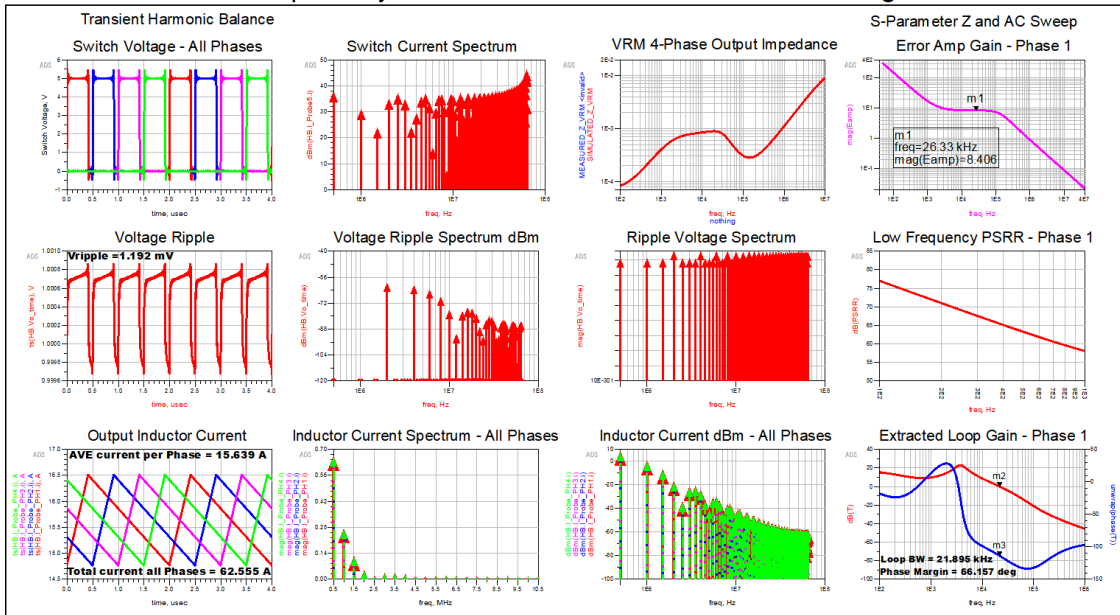State Space Hybrid Model - TPS7H4003 4-PHASE Design




Modeling a 1-phase or N-phase Model is easy





The Voltage Regulator Module (VRM) needs to consider ALL noise sources (large and small signal EMI)


Reverse Transfer - (S12)

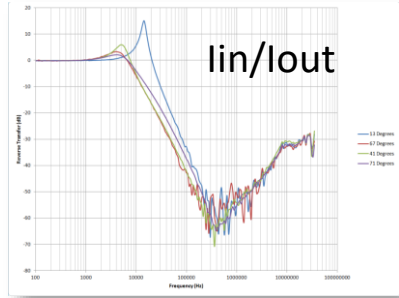

PSRR - (S21)

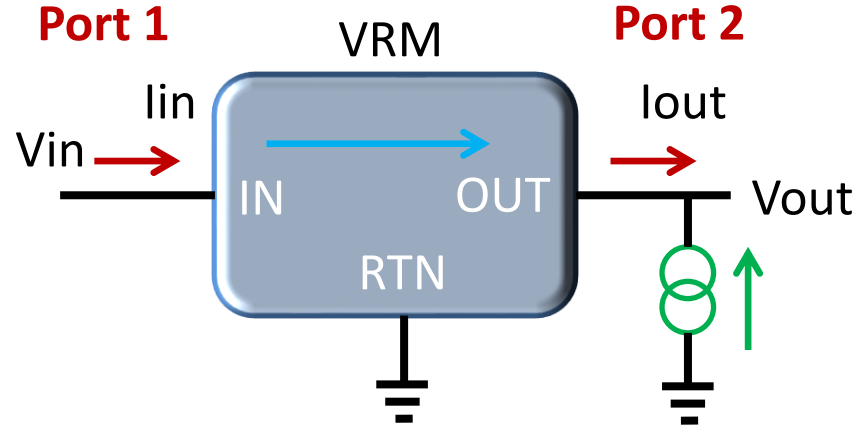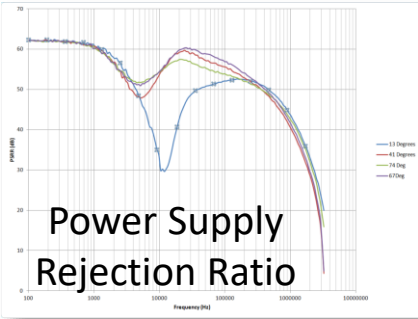

Output Impedance - (S22)

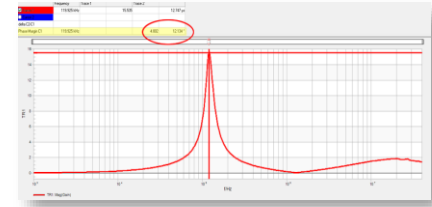


Input Impedance - (S11)



Input impedance can be NEGATIVE!

An R-L model only considers the output impedance

Output Noise/Spikes

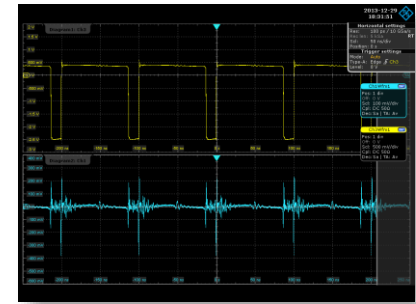

What is a State-Space Average (SSAM) VRM Model

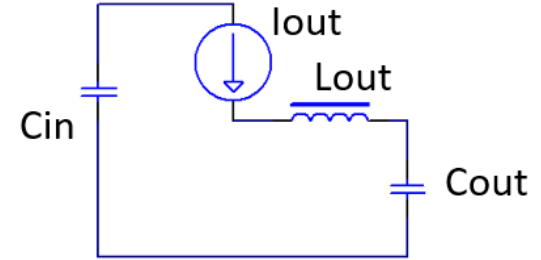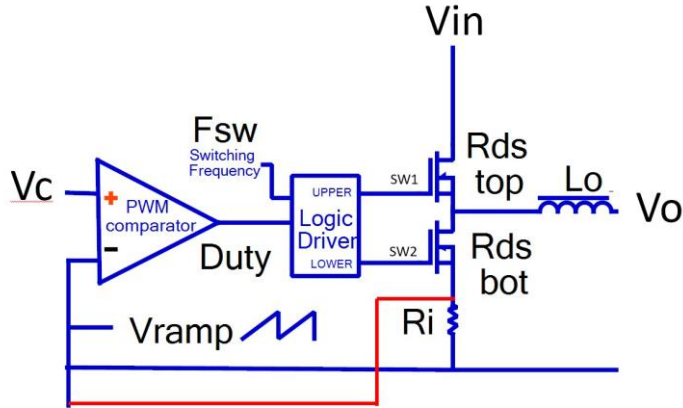

State 1: SW1 = On and SW2 = Off


STATE SPACE AVERAGED MODEL

$$Duty = Ton_{SW1} \cdot Fsw$$

$$Vout = Vin \cdot Duty$$

CURRENT
MODE

$$Iout = k \frac{Vc}{Ri}$$

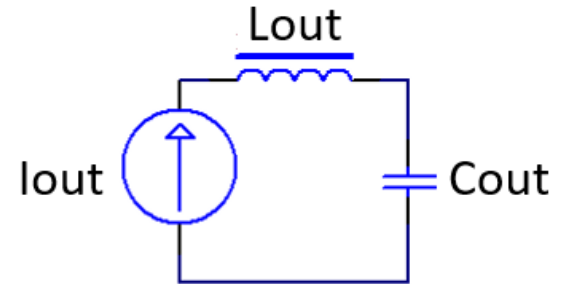

State 2: SW1 = Off and SW2 = On



Why a State-Space Average (SSAM) VRM Model is Better


- Ideal V_{source} has wrong output impedance
- R-L model only models output impedance and not with good accuracy
- RLC model only models output impedance with no information on switching noise, PSRR, stability, etc.
- State Space Average Model does it all and it is measure based and verified for the application.
 - ✓ The math is already done and free to use! Just add the parameters.

	V Source	L-R	L-R-L-R	SSAM
PDN Impedance	INCORRECT RESULT	NOT WELL	REASONABLY	Y
Switching ripple	N	N	N	Y
PSRR/Transients	N	N	N	Y
Negative resistance	N	N	N	Y
Input switching current	N	N	N	Y
Control loop stability	N	N	N	Y
Turn on overshoot	N	N	N	Y
Remote sense	N	N	N	Y




How Bad Can a Simple VRM Model Be?

Model Comparison

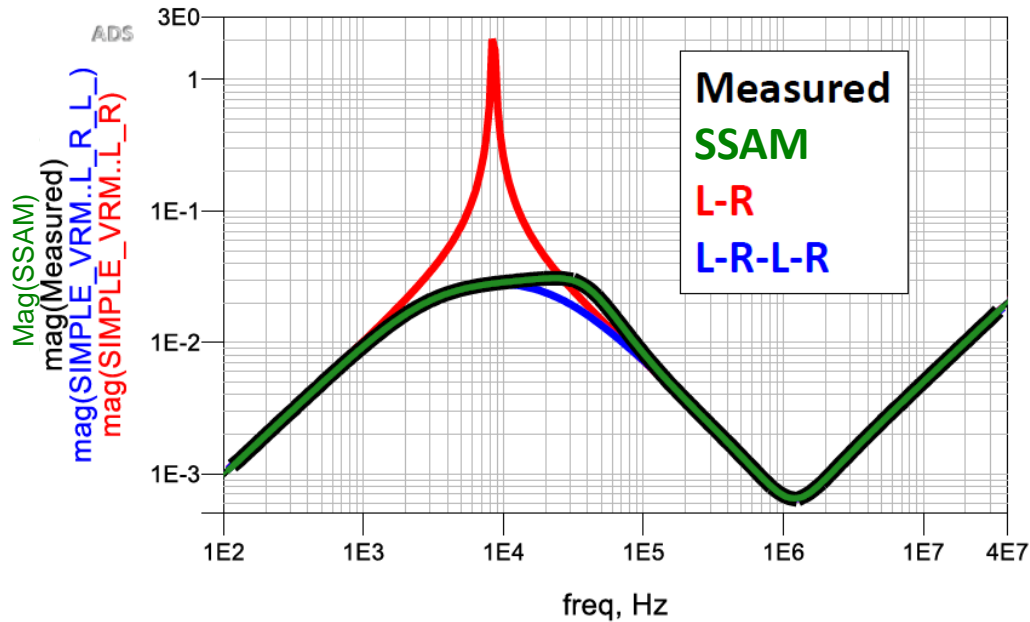


All Noise Sources with an SSAM VRM Model

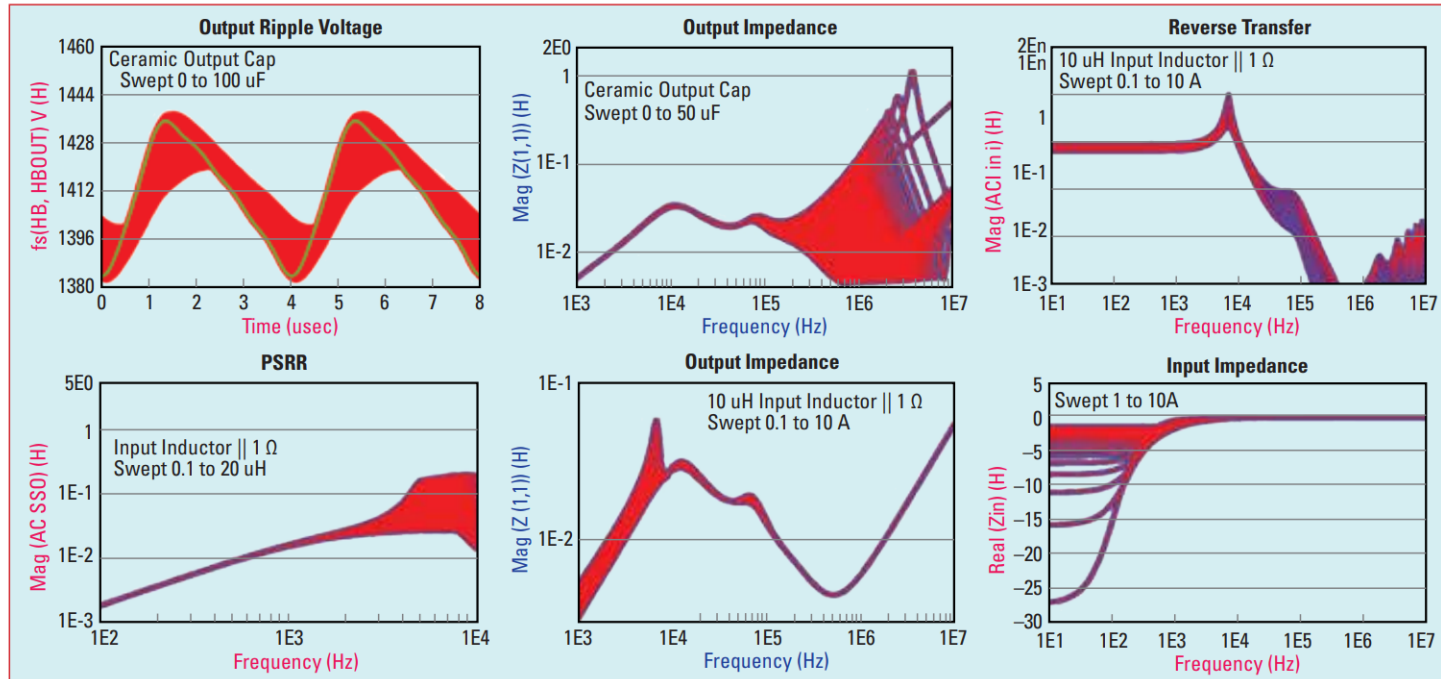State-space average behavioral VRM model predicts performance over process variations.



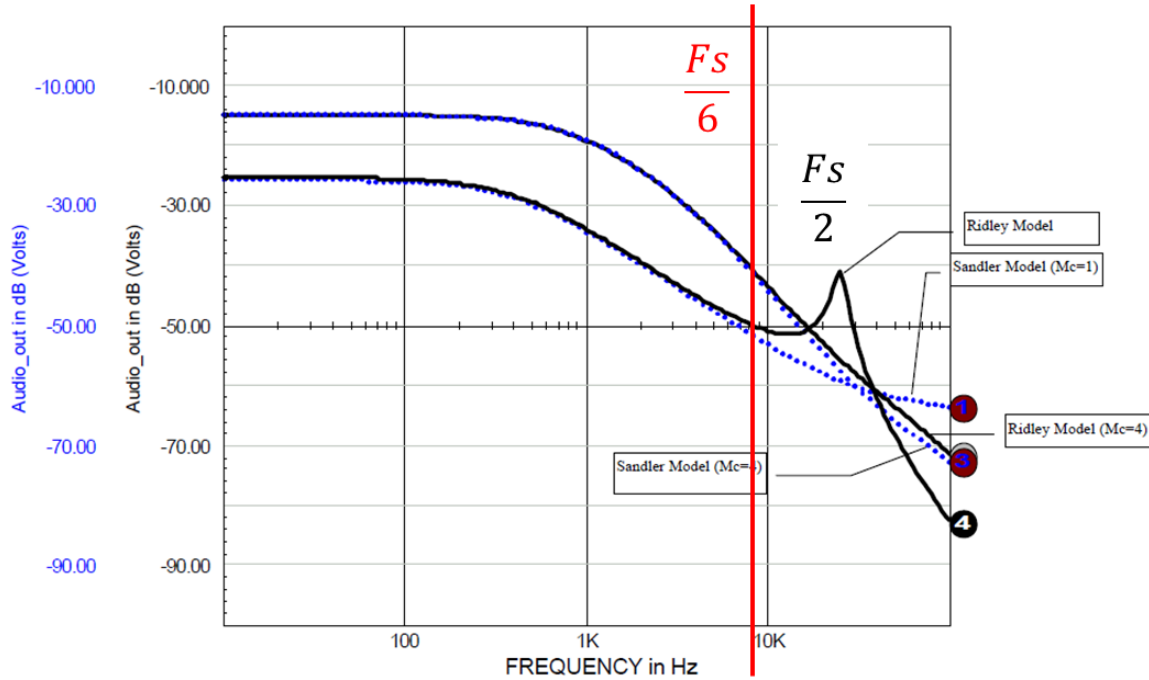
Sandler State-Space Average Model Accuracy: Predicting Audio Susceptibility with Ridley vs. Sandler




Accuracy is reduced for the Sandler State-Space Average VRM Model above $F_s/6$, but accurate where it matters!



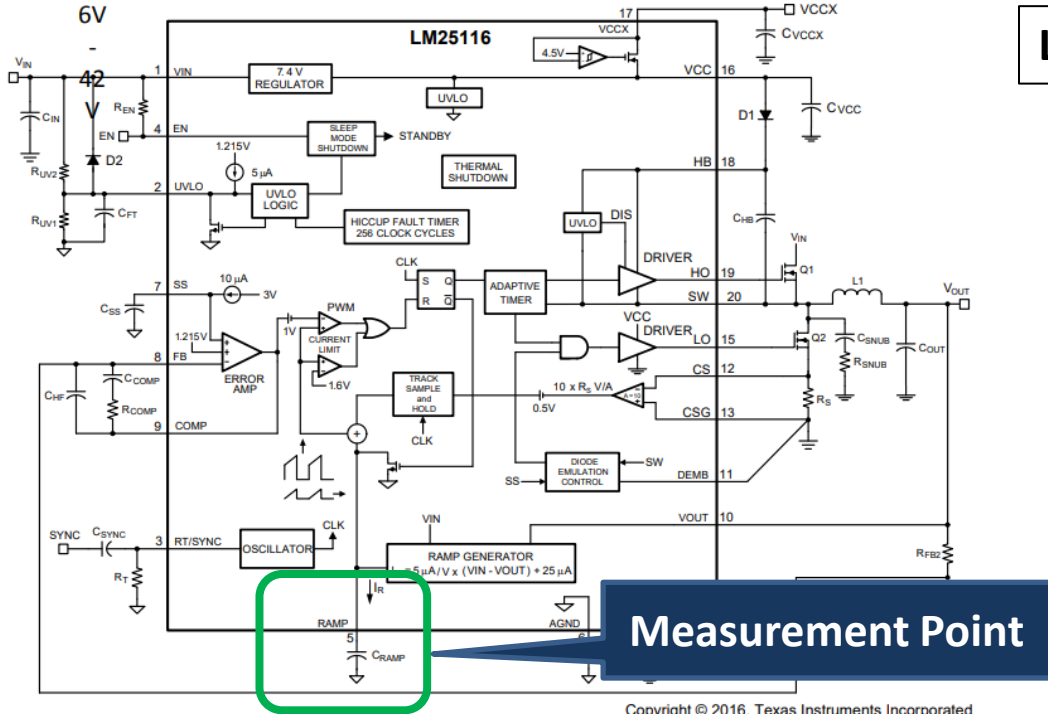SSAM Model Parameters: TI LM25116 VRM V_{RAMP}



LM25116 V_{RAMP} Measurements vs. V_{in}

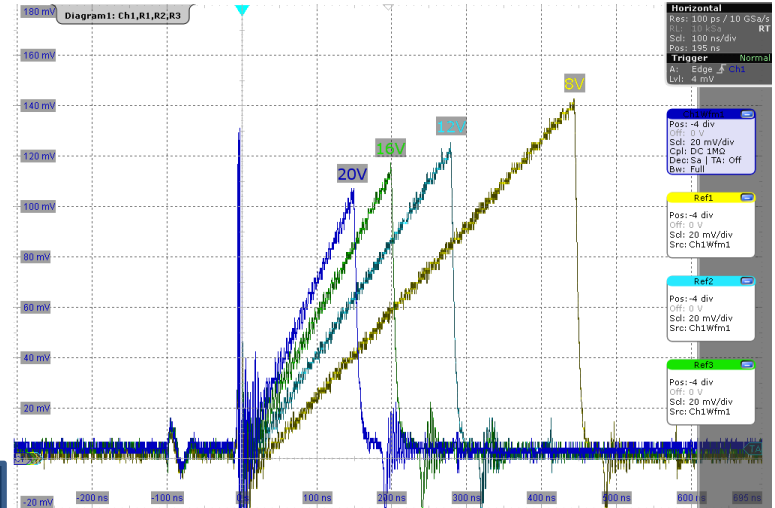

It's not always this easy if you do not have access to V_{RAMP} on the VRM




Sandler State-Space Average Model – Small Signal CCM

S. M. Sandler, *Switch-Mode Power Supply Simulation*, McGraw-Hill, 2005

$$PSRR_{dB} = 20 \log \left| \frac{V_o \cdot (R_i \cdot V_o - 2 \cdot F_{sw} \cdot L_o \cdot V_{ramp})}{R_i \cdot V_{in}^2 - 2 \cdot R_i \cdot V_o \cdot V_{in} + 2 \cdot F_{sw} \cdot L_o \cdot V_{in} \cdot V_{ramp} + 2 \cdot A_v \cdot F_{sw} \cdot L_o \cdot V_{in}} \right|$$
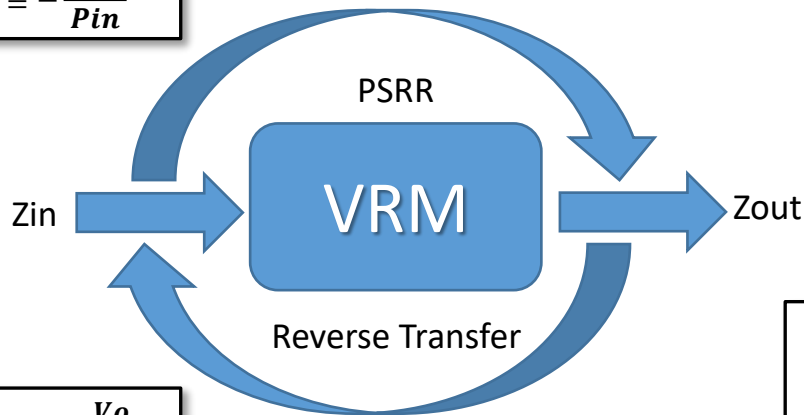
$$R_{in} \cong - \frac{V_{in}^2}{P_{in}}$$



$$Reverse \cong \frac{V_o}{V_{in}}$$

$$\frac{V_o}{V_c} = \frac{2 \cdot F_{sw} \cdot L_o \cdot V_{in}}{R_i \cdot V_{in} - 2 \cdot R_i \cdot V_o + 2 \cdot F_{sw} \cdot L_o \cdot V_{ramp}}$$

$$R_{out} = \frac{2 \cdot F_{sw} \cdot L_o \cdot R_i \cdot V_{in}}{R_i \cdot V_{in} - 2 \cdot R_i \cdot V_o + 2 \cdot F_{sw} \cdot L_o \cdot V_{ramp}} + DCR + RD_{Son}$$

$$= \frac{2 \cdot F_{sw} \cdot L_o \cdot V_{in}}{1 + A_v \cdot \frac{R_i \cdot V_{in} - 2 \cdot R_i \cdot V_o + 2 \cdot F_{sw} \cdot L_o \cdot V_{ramp}}{R_i \cdot V_{in} - 2 \cdot R_i \cdot V_o + 2 \cdot F_{sw} \cdot L_o \cdot V_{ramp}}}$$

$$L_{excess} = \frac{L_o}{1 + \frac{2 \cdot F_{sw} \cdot L_o \cdot V_{in}}{R_i \cdot V_{in} - 2 \cdot R_i \cdot V_o + 2 \cdot F_{sw} \cdot L_o \cdot V_{ramp}} \cdot A_v} + \frac{R_o}{2 \cdot \pi \cdot GBW}$$


Rin and Reverse are insensitive, so less attention is warranted



Now, let's show the process on
an actual VRM of how to
populate the SSAM model



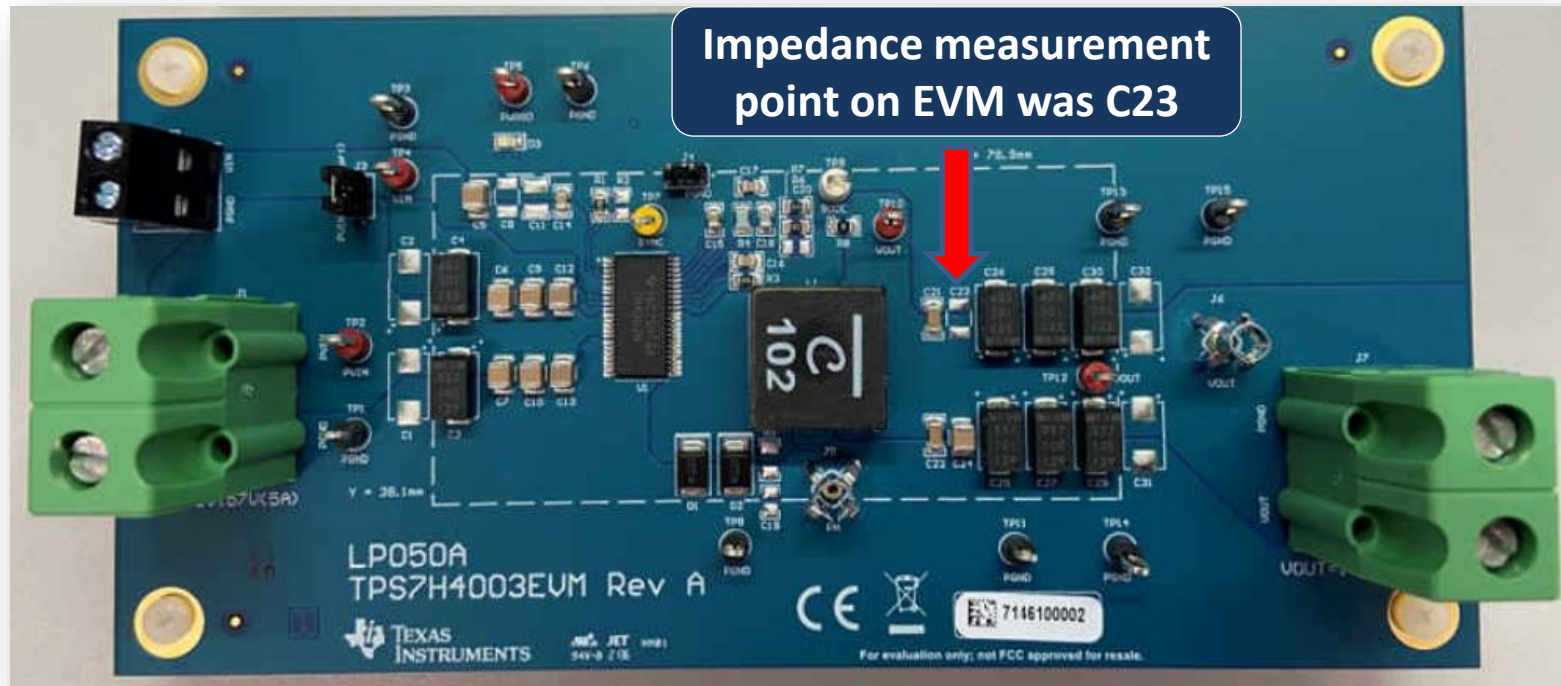Measurement Platform – TI TPS7H4003 Evaluation Module



TPS7H4003 is a radiation tolerant VRM for LEO and GEO applications




Measure Ri Directly on TPS7H4003 VRM

Io	Vcomp
0	0.3274
1	0.3542
2	0.3808
3	0.4078
5	0.4612
6	0.489
8	0.5412
10	0.593

Plot Vcomp vs. Iout results to determine R_i

Measurement Setup

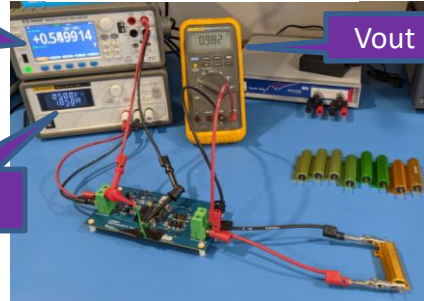


Vcomp result

Vout


VRM Vin

Solder wire on VRM Vcomp pin

Solder point @ C18

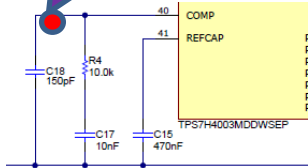
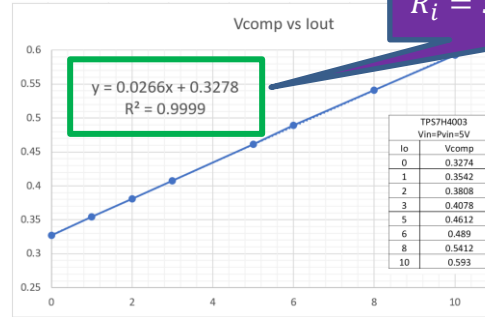
$$R_i = \text{slope} = 26.6 \text{ m}\Omega$$



For R_i we only care about the slope!


This measurement requires a VRM with external Vcomp access

The measured result doesn't always agree with the datasheet



Estimating TPS7H4003 V_{RAMP}

From TPS7H4003 EVAL Schematic

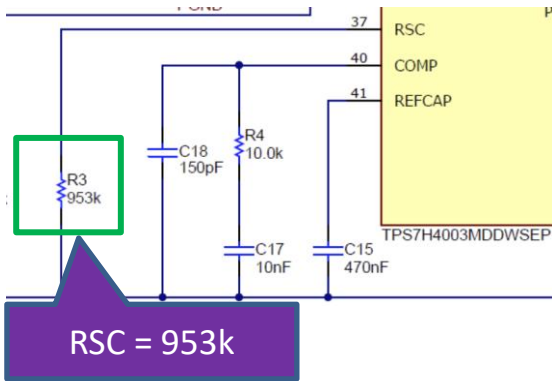

From TPS7H4003 Datasheet

COMP to Iswitch gm ⁽³⁾	COMP = 0.5 V	-55°C	28	38	49	S
		25°C	29	40	50	
		125°C	30	41	52	

Per TPS7H4003 Datasheet

$$RSC = \frac{24000}{f_{sw}} + \frac{1040}{SC} - 30$$

$$R_i = 1/40 = 25 \text{ m}\Omega$$

Solve for Slope Comp (SC)

TPS7H4003 $f_{sw} = 500 \text{ kHz} \rightarrow SW_period = 2\mu\text{s}$ period

$$SC = 1.1A/\mu\text{s} \tag{1}$$

$$SC_{per \text{ duty cycle}} = SC \cdot SW_{period} = 1.1A/\mu\text{s} \cdot 2\mu\text{s} = 2.2A/100\% \text{ duty cycle} \tag{2}$$


$$V_{RAMP} = SC \cdot R_i = 2.2A \cdot 0.025\Omega = 0.055V \tag{3}$$

VRM vendors do not always make this information available to populate the model




Simulating the Open Loop Plant Gain

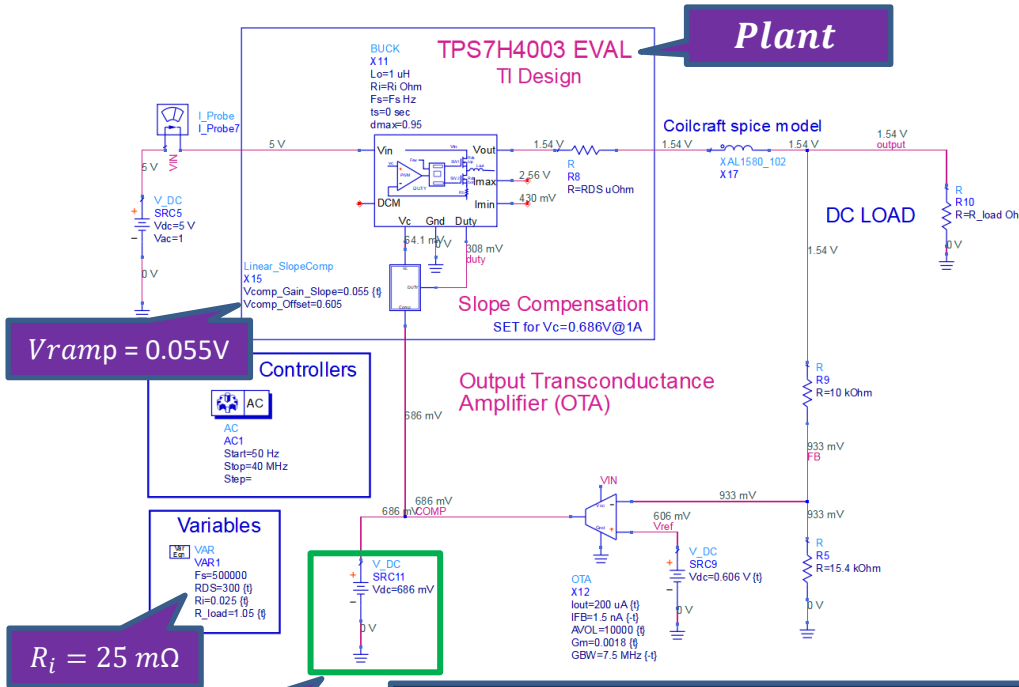Showing Plant Open Loop Gain using datasheet V_{ramp} and R_i Values



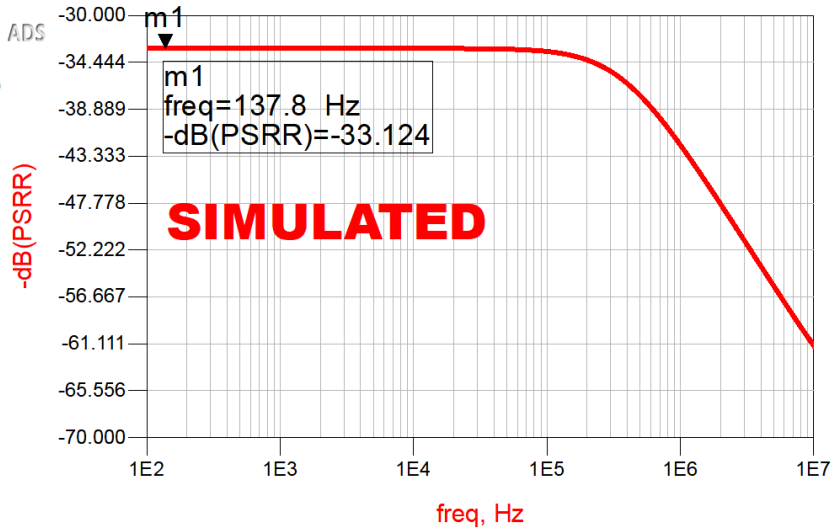TPS7H4003 Open Loop PSRR
5Vin, 1Vout, 1A Load




Fixed Feedback Vcomp for a given load



PSRR Setup with the TPS7H4003

Let's measure the open loop plant gain and closed loop PSRR


Bode 100

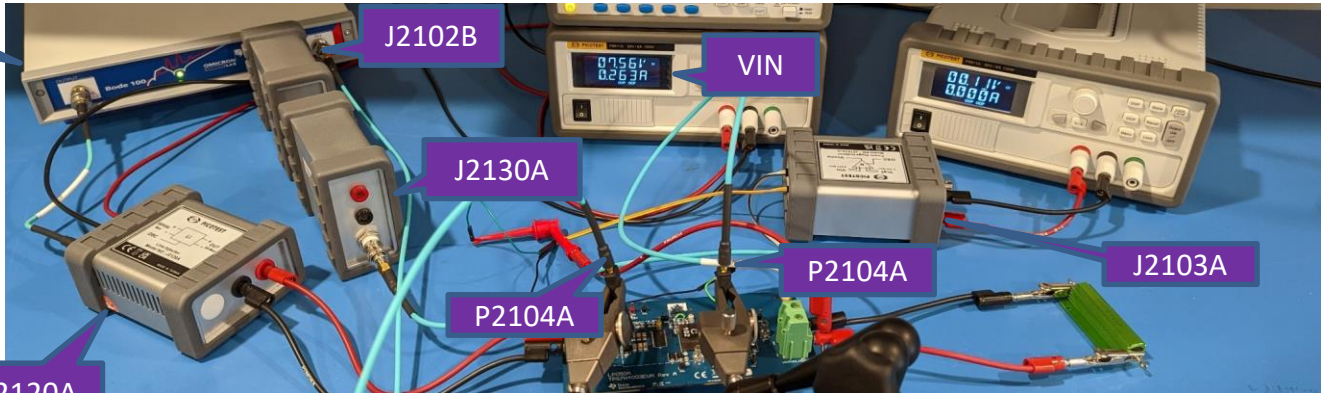

Now, let's
measure this!


CH2 - VIN

CH1 - VOUT

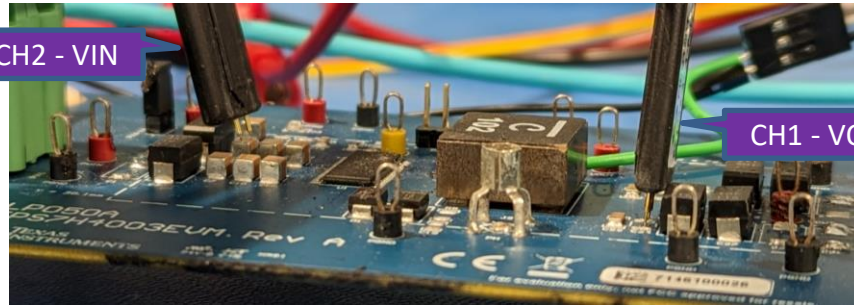


Open Loop PSRR – TPS7H4003 Gain Magnitude and Phase

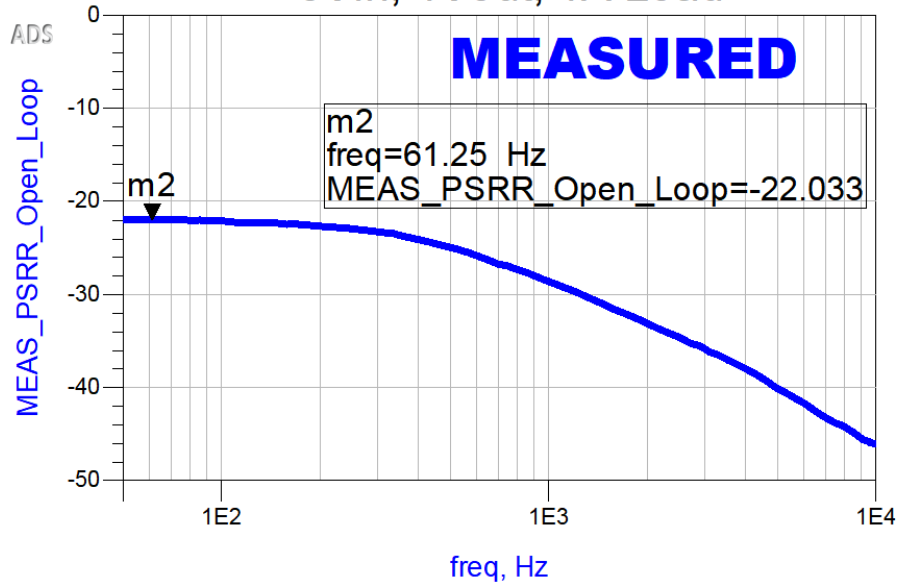TPS7H4003 Open Loop Gain 5Vin, 1Vout, 1A Load




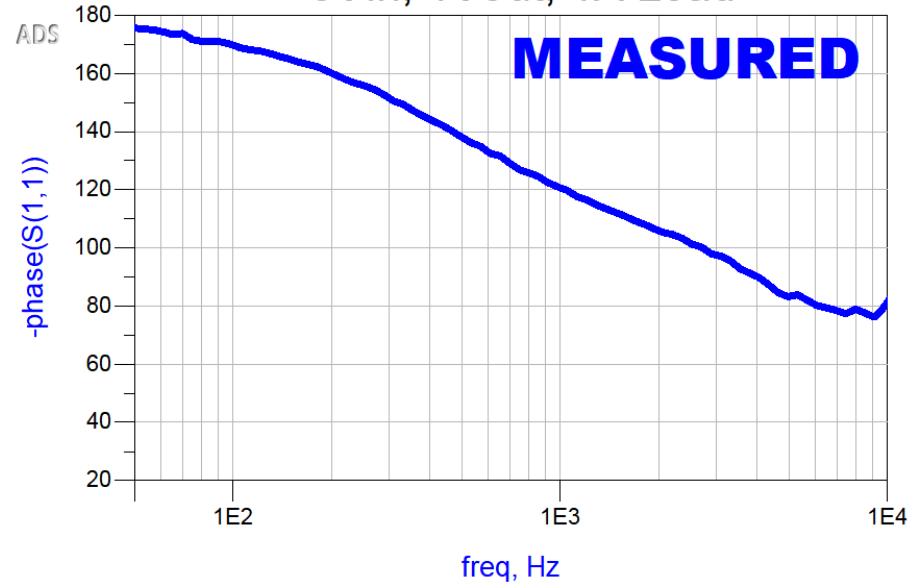TPS7H4003 Open Loop Gain Phase 5Vin, 1Vout, 1A Load




Measuring PSRR TPS7H4003 Open and Closed Loop

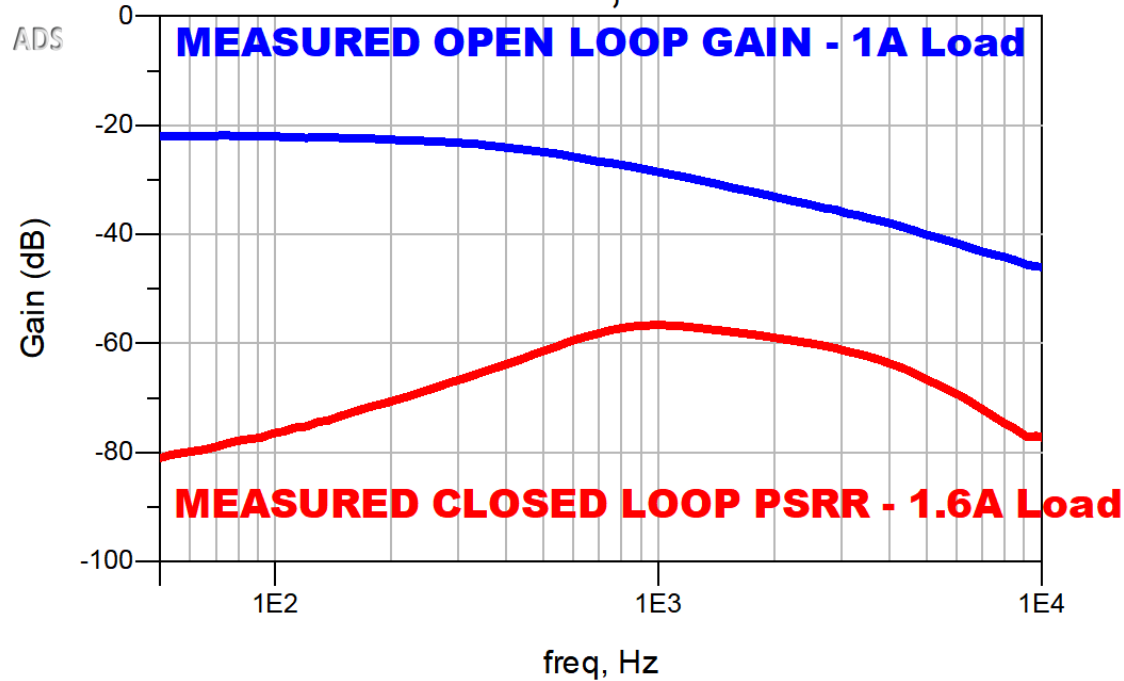TPS7H4003 PSRR Open Loop vs. Closed Loop Gain 5Vin, 1Vout



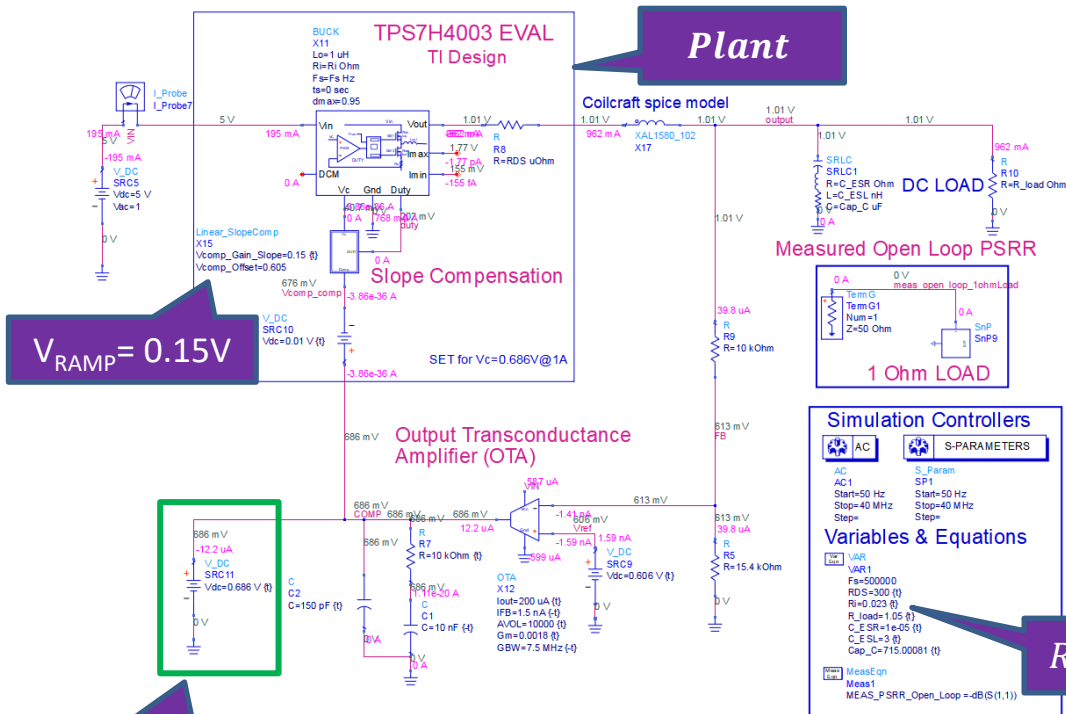PSRR changes with load, so measure Open Loop




$V_{RAMP} = 0.15V$



$R_i = 23\ m\Omega$

After tuning to match measurement, $V_{RAMP} = 0.15V$

TPS7H4003 Open Loop PSRR

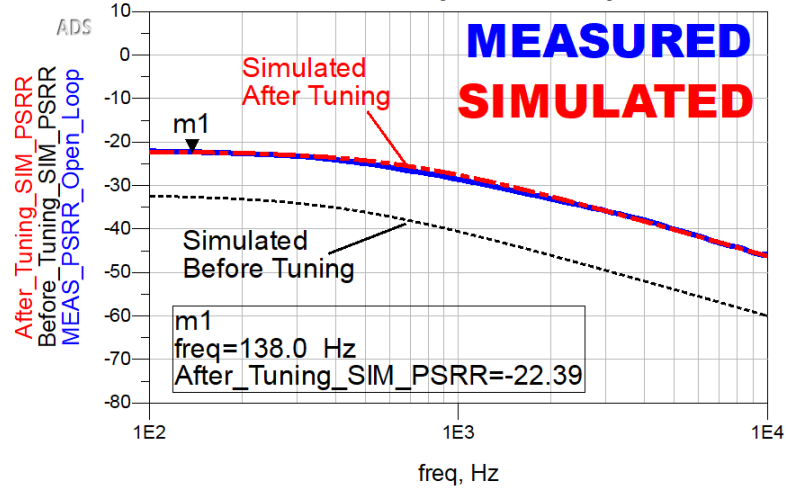

Measuring VRM Output Impedance

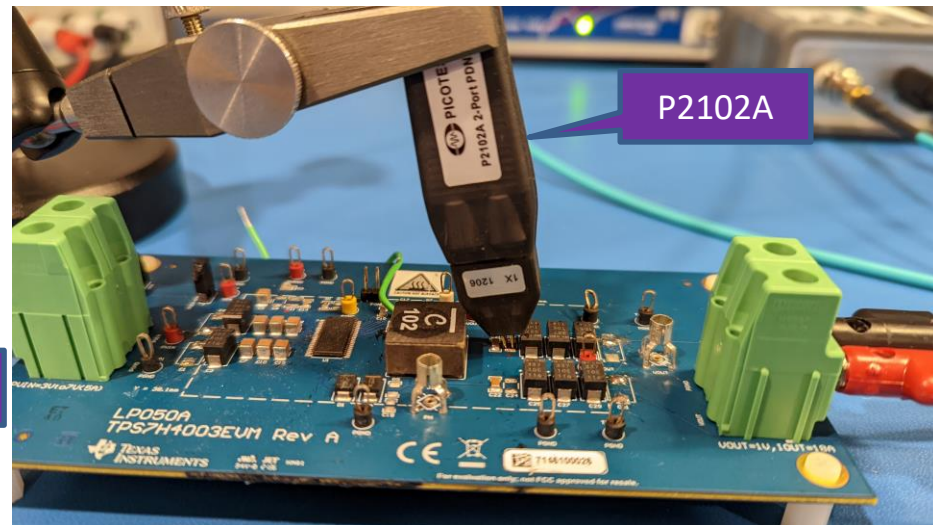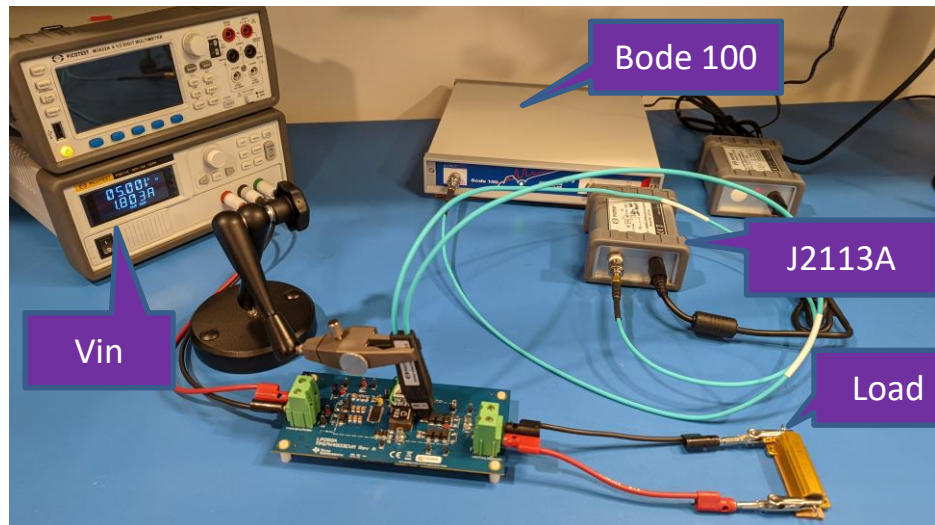

Measure the VRM ON and OFF impedances


When doing a 2-port impedance measurement, it is important to remove the capacitor to prevent AC coupling between the 2 ports on the probe, which can cause measurement error



Why use the Harmonic Balance Simulator with SSAM


- Fourier Theory says time domain waveforms are made up of frequency domain waveforms.
- Solving a circuit in the Frequency Domain can be much faster since it limits the frequencies and jumps to steady state.

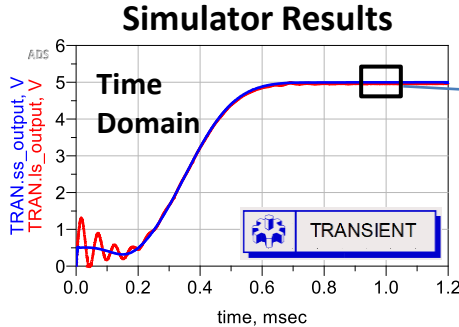Transient must reach steady state to measure ripple.
50,000 time-steps!




Time Domain
Transient Sim
 Wait for Steady State
 Minutes, Hours, **Days**


Steady State Ripple vs. Time

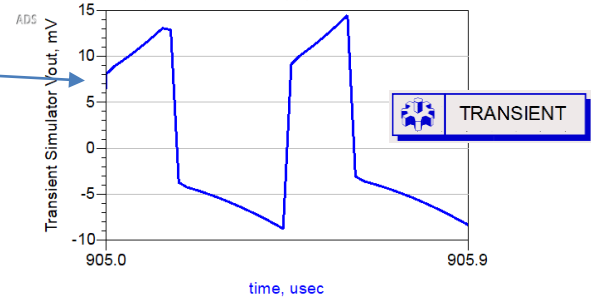

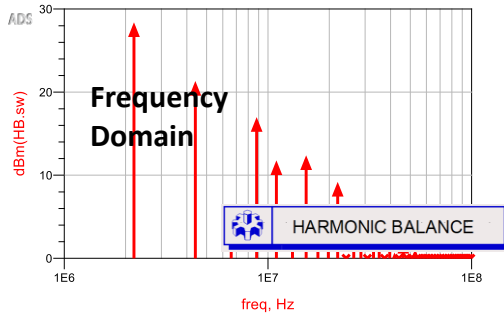Harmonic Balance simulates harmonics of the switching frequency.
Only 255 Frequencies for steady state ripple!



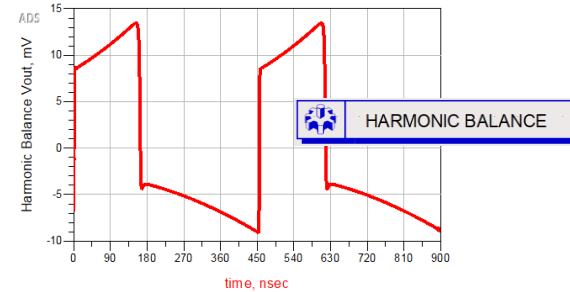Frequency Domain
Harmonic Balance Sim
 FFT jumps to Steady State
Seconds, Minutes, Hours



Data shown is for one VRM, typical PCB design has dozens of VRMs




State-Space Average Model TPS7H4003 EVM – TI Design

Does not include PCB effects

Put it all together in the Sandler SSAM VRM Model



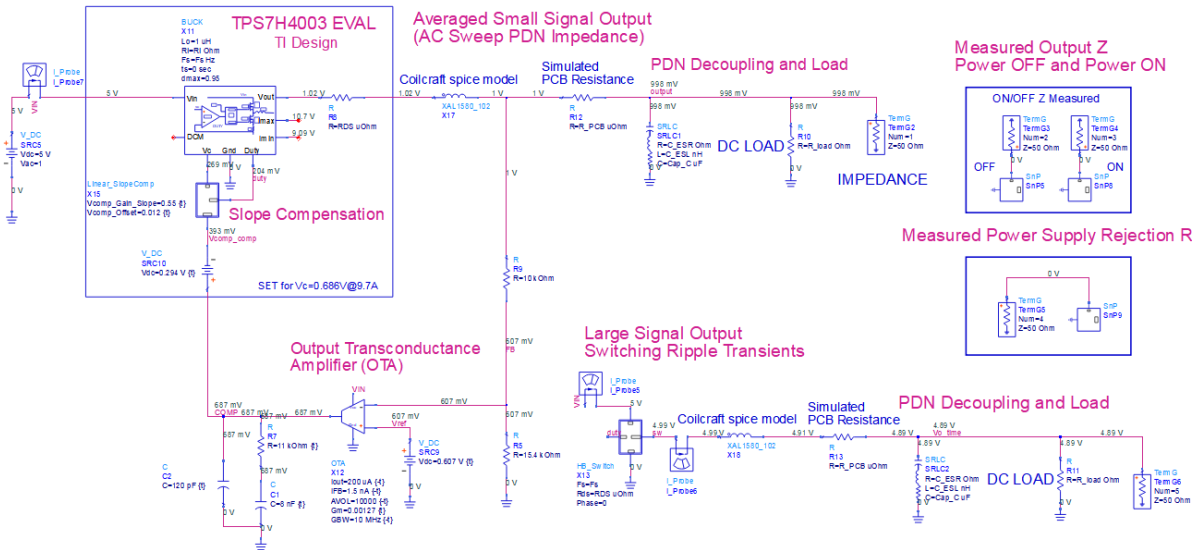Small Signal Hybrid State Based Averaged VRM Model Including Discontinuous and Continuous Mode (DCM) Operation



Tuned Variables for Matching VRM Model with Measurement

Variables

VAR	VAR1
Fs	=100000
RDS	=1000 (Ω)
RH	=220 (Ω)
RL	=1000 (Ω)
CE	=1000000 (F)
CE2	=1000000 (F)
CE3	=1000000 (F)
CE4	=1000000 (F)
CE100	=1000000 (F)

Three Separate Simulations in one Schematic

Simulation Controllers

AC	S-PARAMETERS	HARMONIC BALANCE
AC	S_PARAM	HARMONIC_BALANCE
AC1	SP1	HB1
Start=500 Hz	Start=500 Hz	Order=128
Stop=10 MHz	Stop=10 MHz	Order=128
Step=	Step=	Order=128

Equations

```

MEASUREMENT
M8961
SIMULATED_Z_VRM=avg(Z(1,1))
MEASURED_Z_VRM=avg(Z(2,3))
MEASURED_PDRR=avg(P(4,4))
    
```





TPS7H4003 State-Space Average Model Results



Does not include PCB effects

Simulation matches measurement...
Model is good!

We're finished!
Or are we?

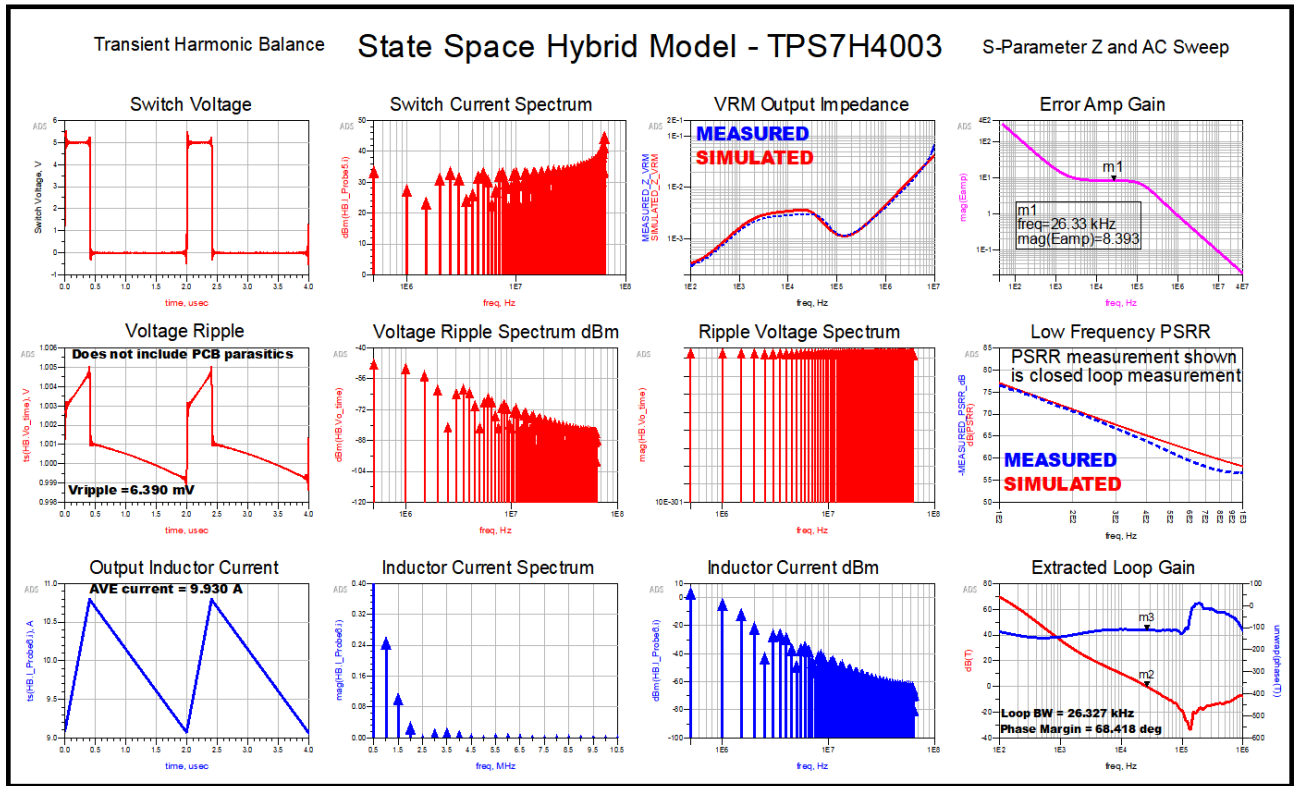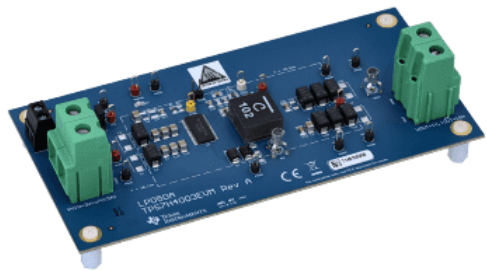

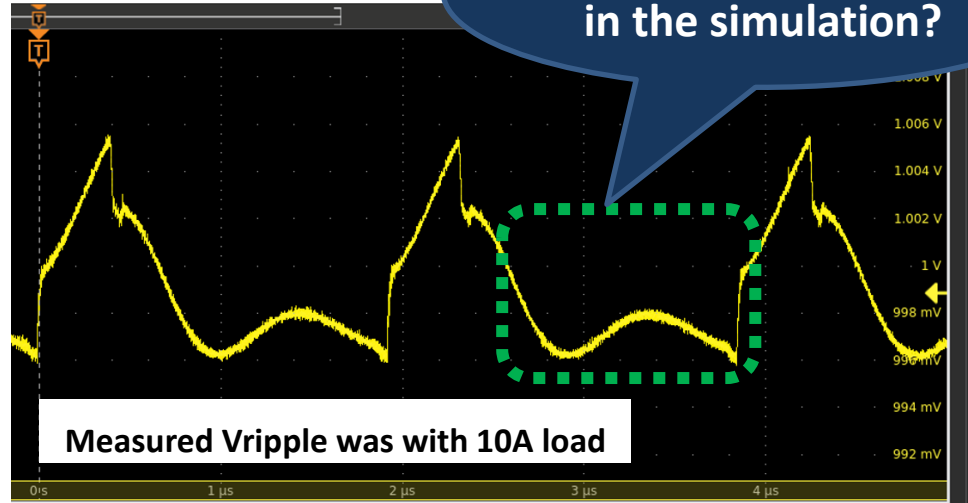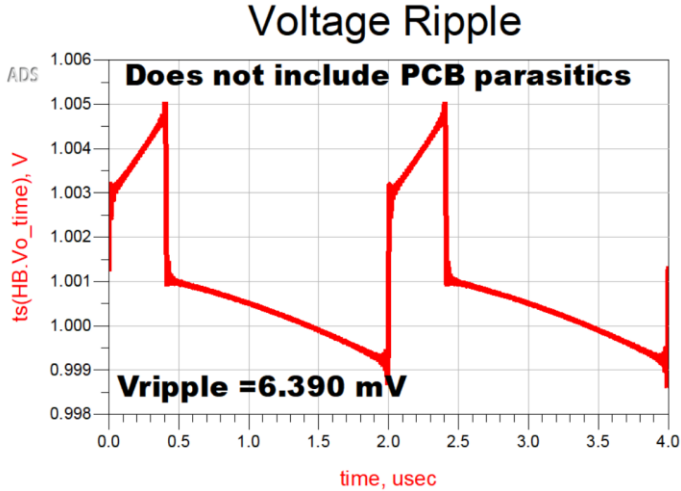TPS7H4003 VRM Output Voltage Ripple Simulation vs. Measurement



Comparing the simulated voltage ripple to the measurement


Measurement point



State-Space Average VRM Model TPS7H4003 EVM – TI Design


Does include PCB effects

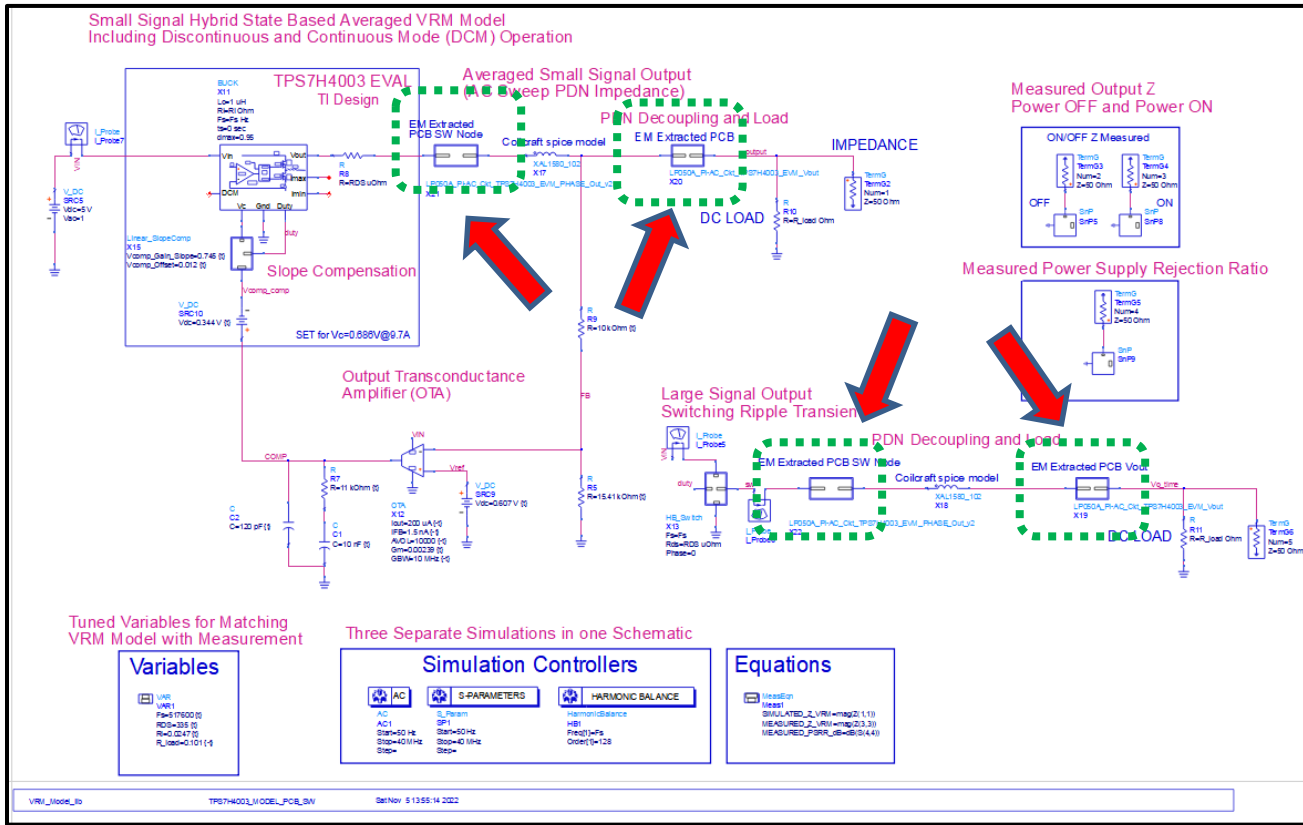Let's add the PCB effects to our model and see what happens to the voltage ripple




TPS7H4003 VRM Output Voltage Ripple

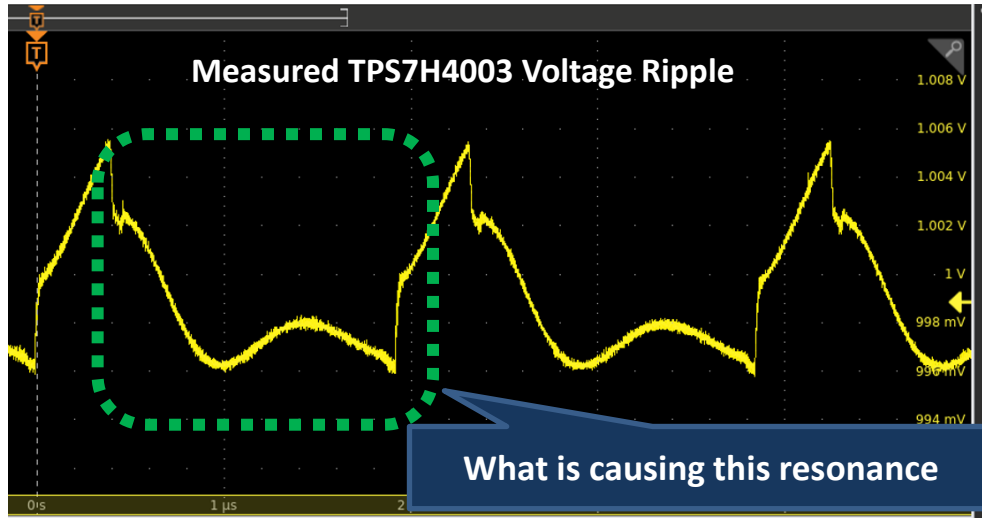Measurement vs. Simulation with included PCB effects




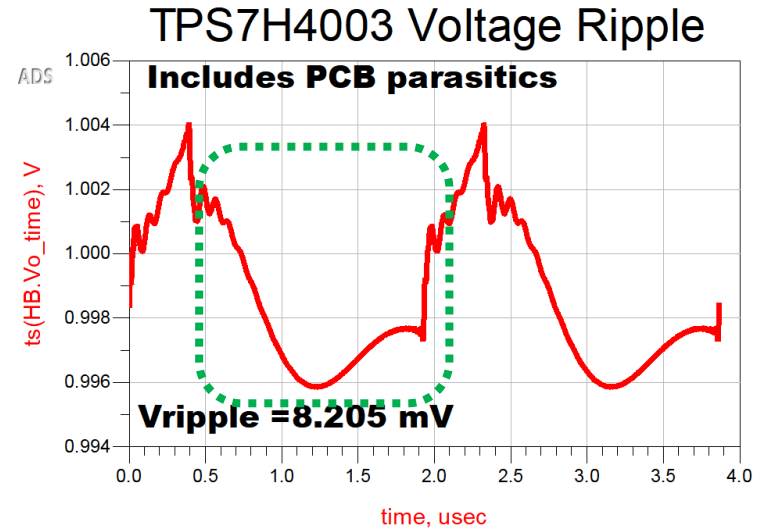Simulated TPS7H4003 Voltage Ripple using State-Space Average VRM Model




All extracted PCB artwork was from Keysight PathWave PIPro

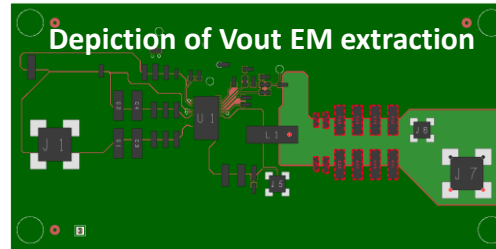Extracted PCB Artwork, the extracted Switch node is not depicted




Exploring the PCB Effects seen in the Output Ripple

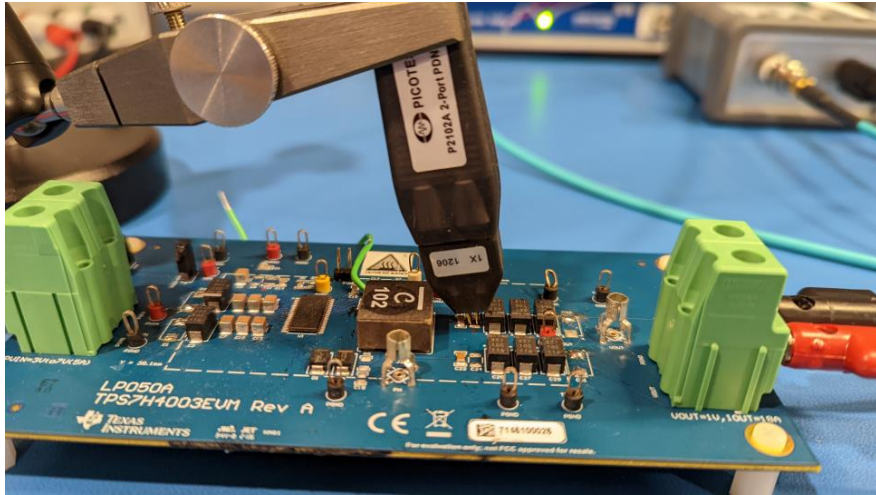Output Impedance Measurement Setup with 2-port PDN Probe



Measurement Point at C23


Measured VRM Output Impedance

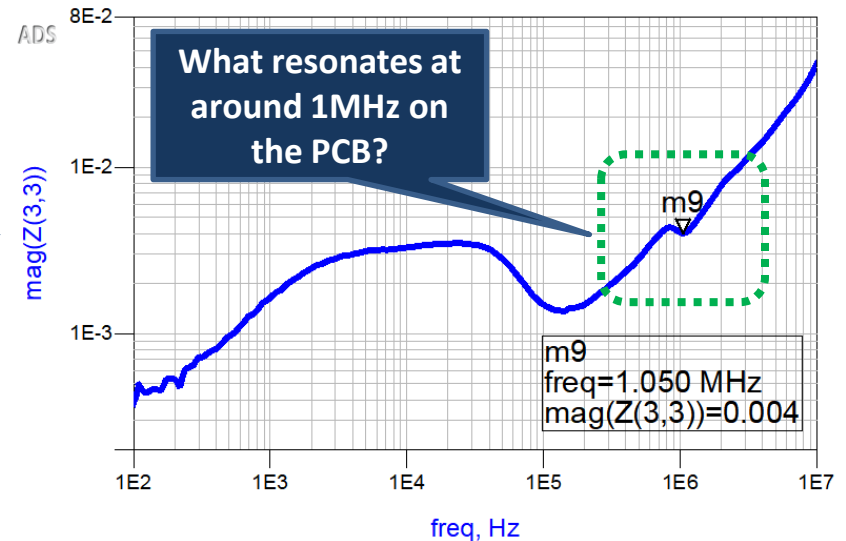

Output impedance measurement shows 1MHz resonance


TPS7H4003 VRM – Investigating the Current Density on the PCB

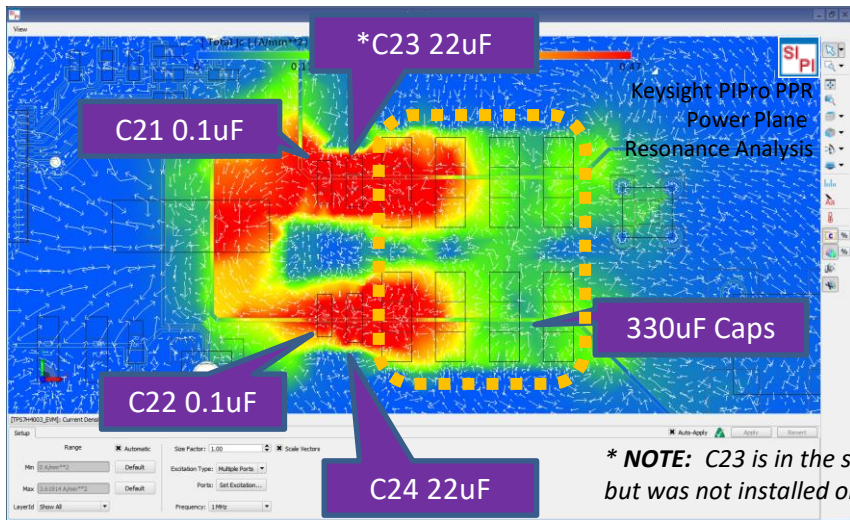Current Density Plot is created with 1MHz Resonance Frequency



22 uF Cap resonances at 1 MHz!

22uF Capacitor Output Impedance

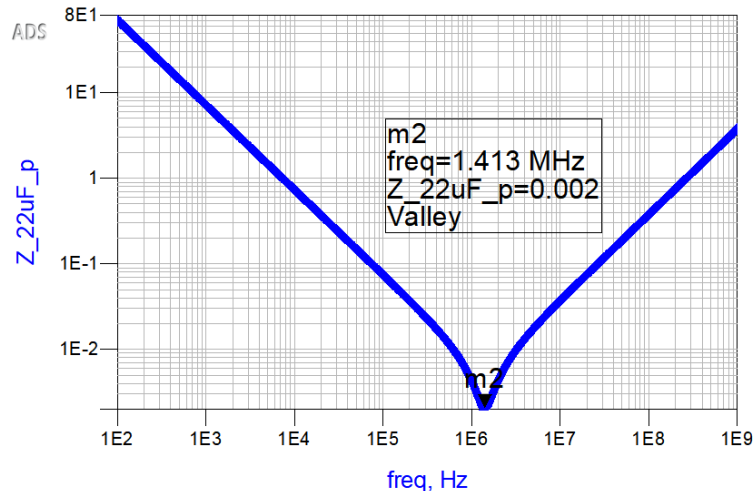

Multiple Caps are resonating at 1MHz, but only one is the culprit

Further Analysis 22uF vendor spice model confirms C24 is the potential resonance point on the PCB....


The 22uF Cap (C24) looks be our problem, right?




TPS7H4003 VRM – Removing the 22uF Capacitor

Simulated Vripple with 9.8A load

TPS7H4003 Voltage Ripple

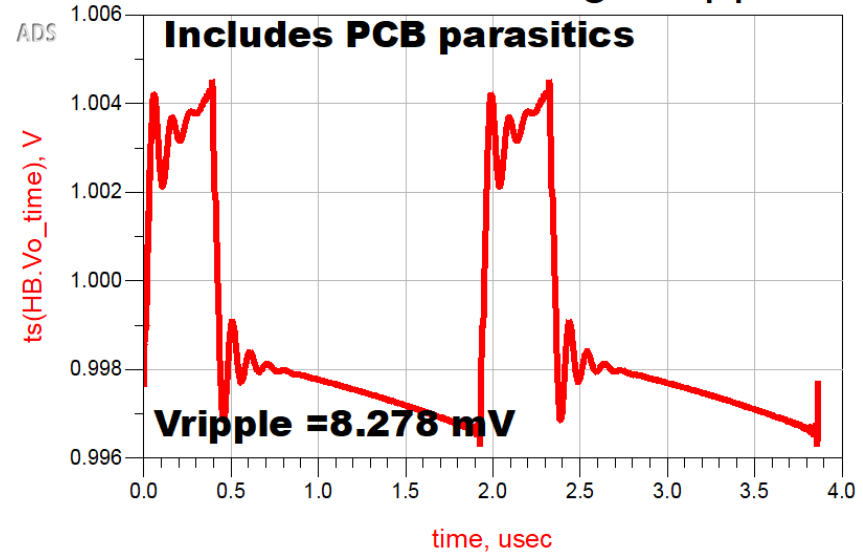

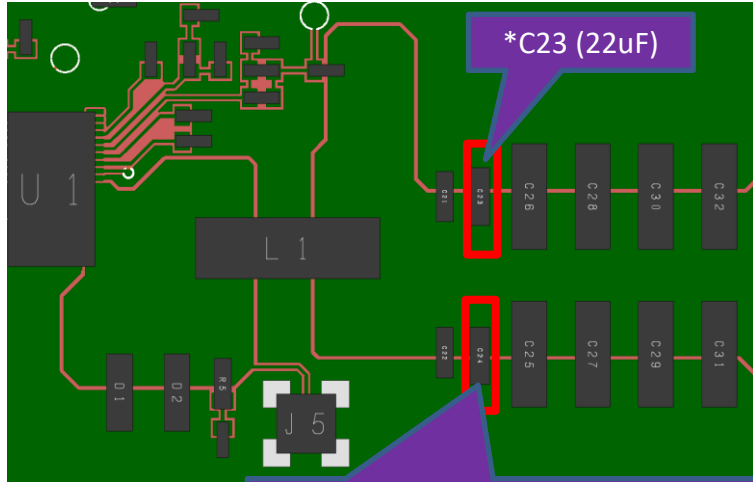What happens if we remove the 22uF cap (C24)?



Removed C24 (22uF) cap
*Note: C23 was already removed.

Removing a single capacitor removed the resonance seen in the output voltage ripple!

Simulating with PCB effects matters for getting the answer right.




Fine Tuning the TPS7H4003 EVM SSAM VRM Model – Digital Twin

Voltage Ripple - TPS7H4003 VRM EVAL PCB

Measurement vs. Simulated State Space Average Model

$$\approx \Delta I_L \cdot ESR$$

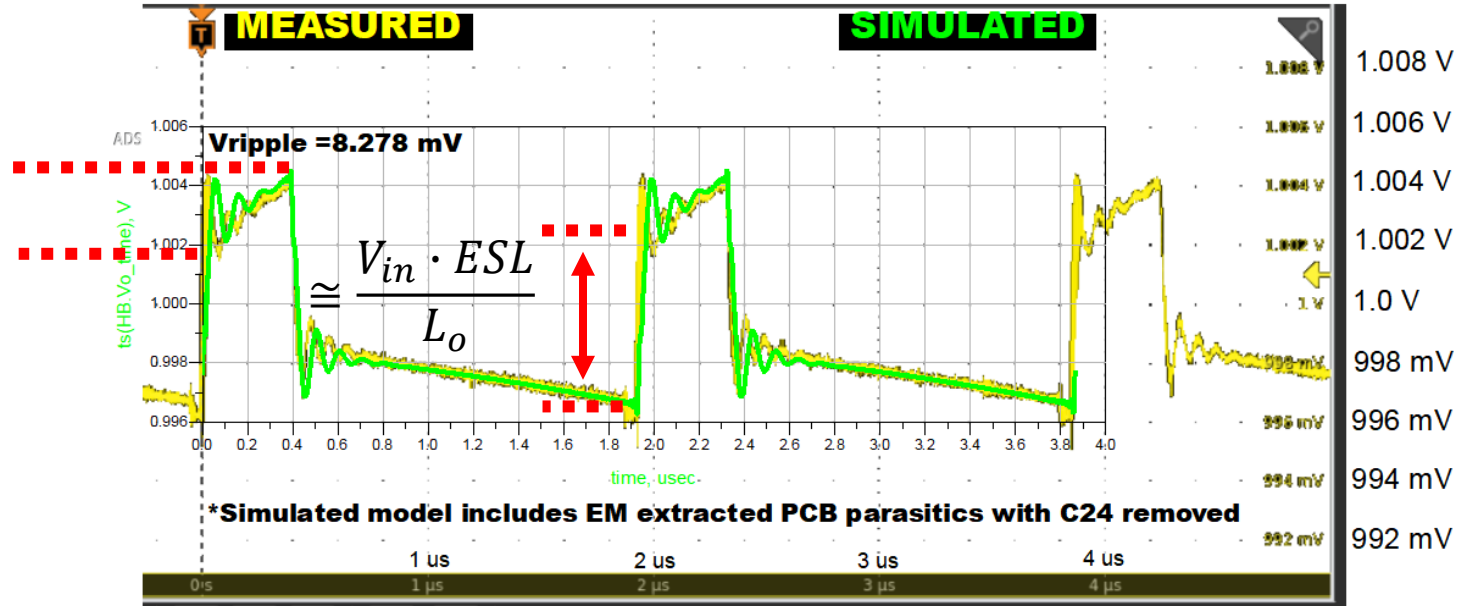


The model accurately matches the measurement





The Voltage Regulator Module (VRM) needs to consider ALL noise sources (large and small signal EMI)

Reverse Transfer - (S12)

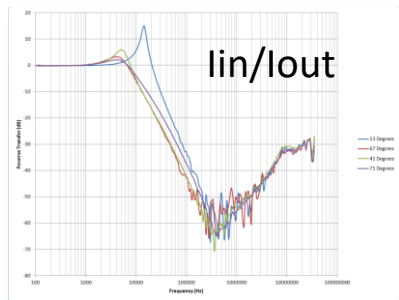

PSRR - (S21)

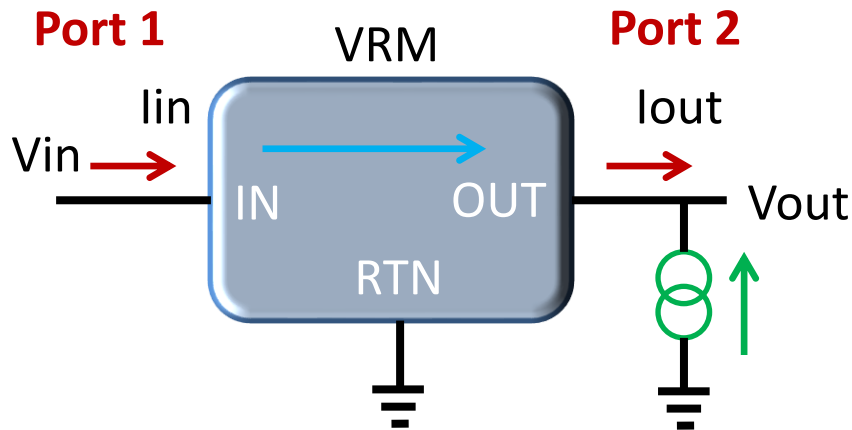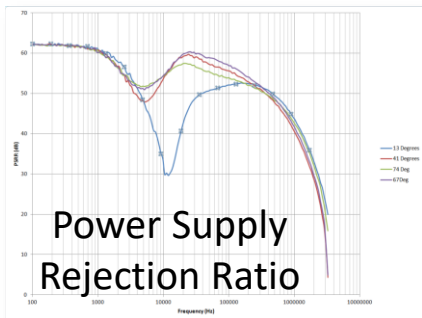


Input Impedance - (S11)


Input impedance can be NEGATIVE!

An R-L model only considers the output impedance

Output Impedance - (S22)

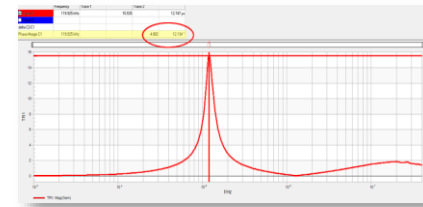


Output Noise/Spikes

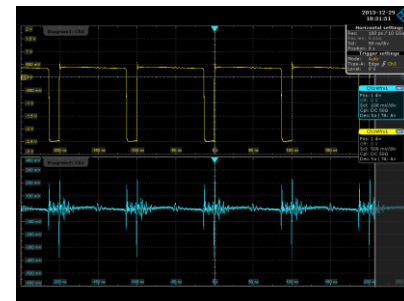

Evaluating the Results.. How much better is the SSAM VRM Model?


Model Comparison

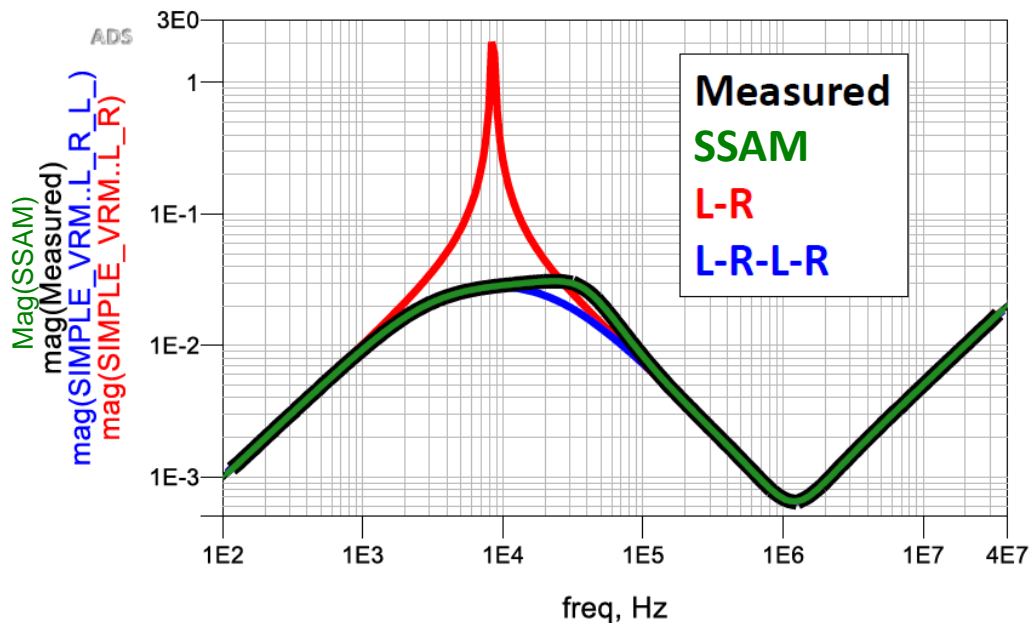


TPS7H4003 Measurement vs. Fitted Passive Spice Model

How much do we care about simulation with the PCB effects with the State-Space Average Model?

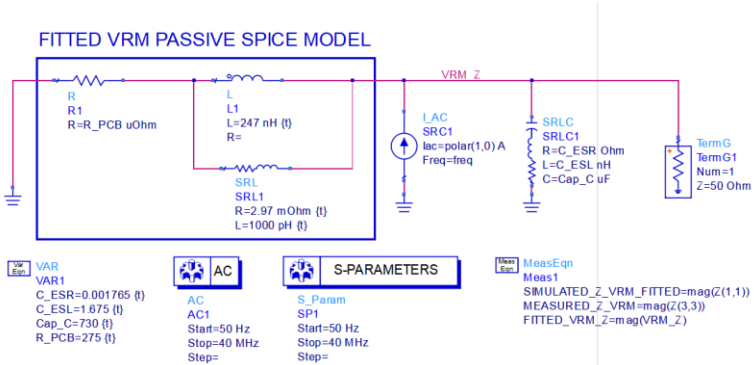To answer that question, we need to first create a fitted passive spice VRM model




Measured Output Z
Power OFF and Power ON

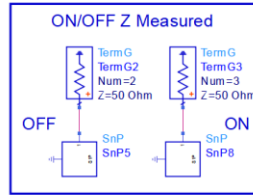

MEASURED_Z_VRM
SIMULATED_Z_VRM_FITTED

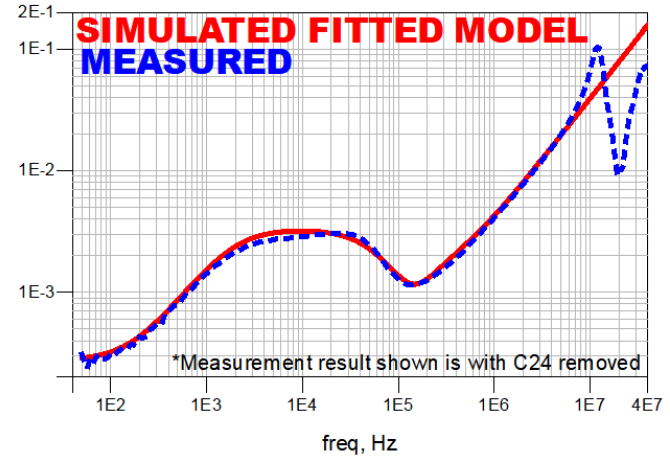TPS7H4003 EVAL
Measurement vs. Fitted VRM Passive Spice Model




TPS7H4003 EVM with PCB SSAM vs. Fitted Passive SPICE Model Step Response

10A, 100nsec step load without PCB effects

Comparing the step response between the State-Space Average Model and the Fitted Passive Spice VRM model

VRM Output Impedance

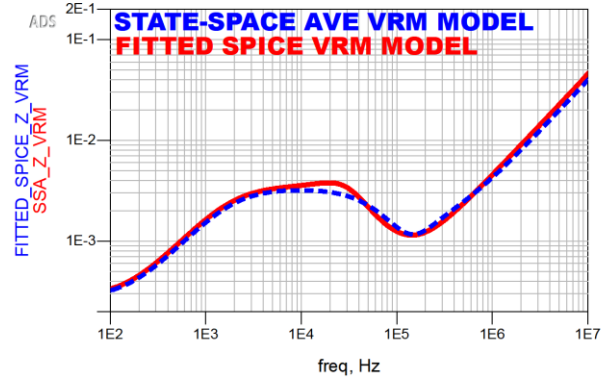
State-Space Average VRM vs. Fitted Passive Spice VRM Model



Output Impedance Correlates between both models

TPS7H4003 EVAL

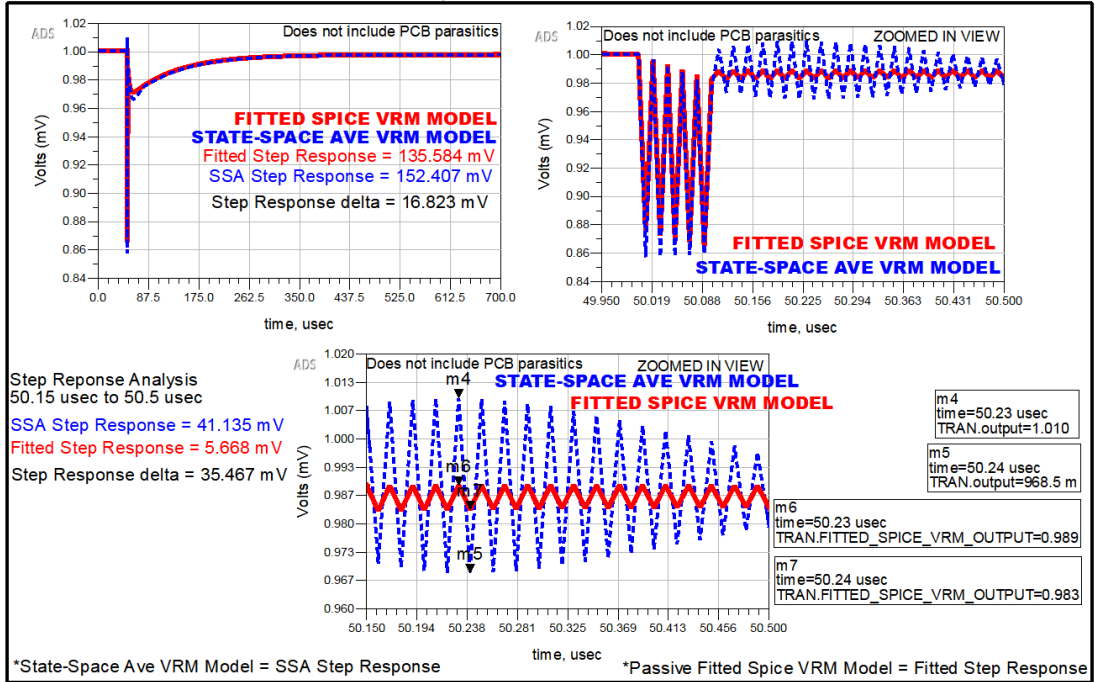VRM Step Load Response - State-Space Ave VRM vs. Fitted VRM Spice Model
 Step Load = 10A, 100 nsec rise time



86% Change in transient step response between both models without PCB Effects



TPS7H4003 EVAL with PCB SSAM vs. Fitted Passive Spice Model Step Response


10A, 100nsec step load with PCB effects

TPS7H4003 EVAL with PCB
 VRM Step Load Response - State-Space Ave VRM vs. Fitted VRM Spice Model
 Step Load = 10A, 100 nsec rise time

41% change in transient response from SSAM VRM model

Now let's include the PCB effects and compare the results again

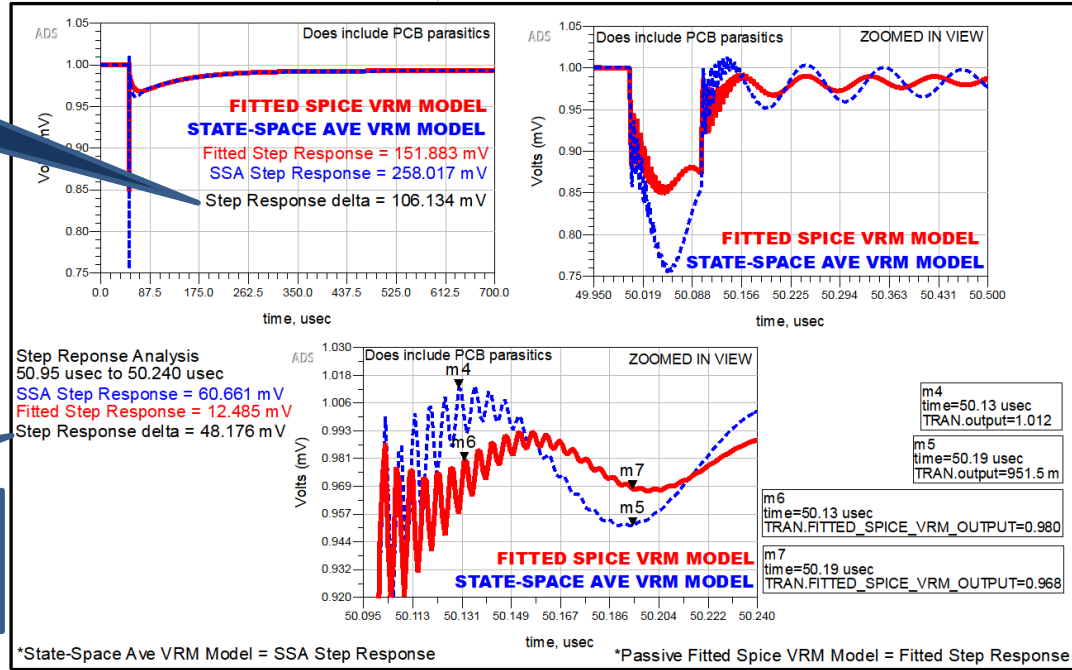79% change in transient response from SSAM VRM model




79% Change in transient step response between both models with PCB Effects



TPS7H4003 EVM with PCB SSAM vs. Fitted Passive Spice Model Noise Spectrum from Step Response 10A, 100nsec step load without PCB effects

TPS7H4003 EVAL without PCB

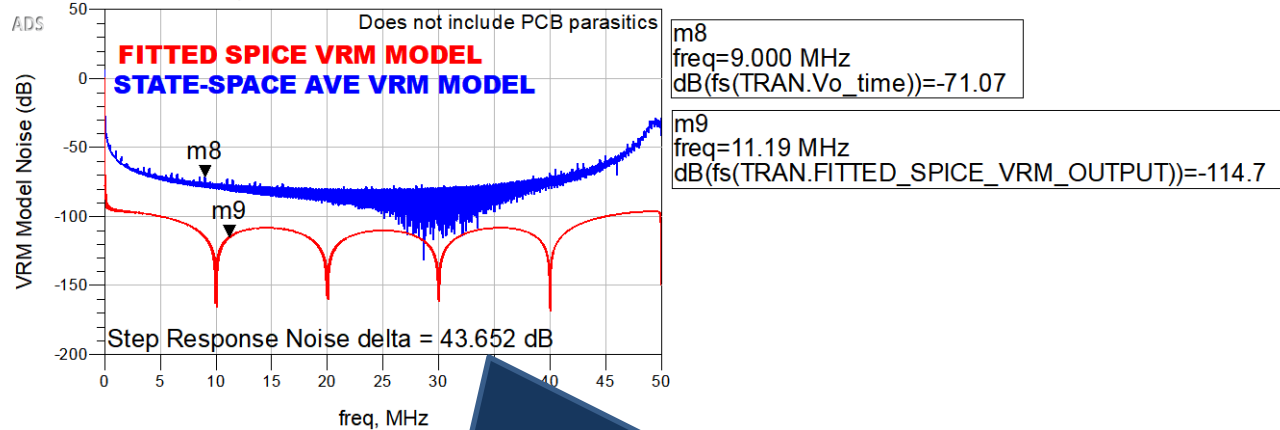VRM Noise Spectrum from Step Load - State-Space Ave VRM vs. Fitted VRM Spice Model
Step Load = 10A, 100 nsec rise time



Let's compare the results in the noise spectrum without the PCB effects

61.42% (44 dB) change in noise spectrum from SSAM

61% (44 dB) Change in transient step noise spectrum response between both models without PCB Effects




TPS7H4003 EVM with PCB SSAM vs. Fitted Passive Spice Model Noise Spectrum from Step Response 10A, 100nsec step load with PCB effects

TPS7H4003 EVAL with PCB

VRM Noise Spectrum from Step Load - State-Space Ave VRM vs. Fitted VRM Spice Model

Step Load = 10A, 100 nsec rise time

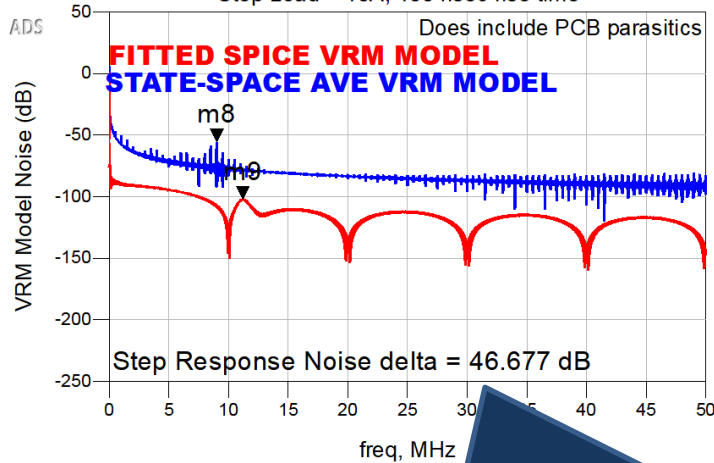

m8
freq=9.000 MHz
dB(fs(Vo_time))=-55.33
Peak

m9
freq=11.19 MHz
dB(fs(FITTED_SPICE_VRM_OUTPUT))=-102.0
Peak

Now let's include the PCB effects and compare the results in the noise spectrum


84% (47 dB) change in noise spectrum from SSAM

84% (47 dB) Change in transient step noise spectrum response between both models with PCB Effects




.....And Picotest NISM works in ADS also!

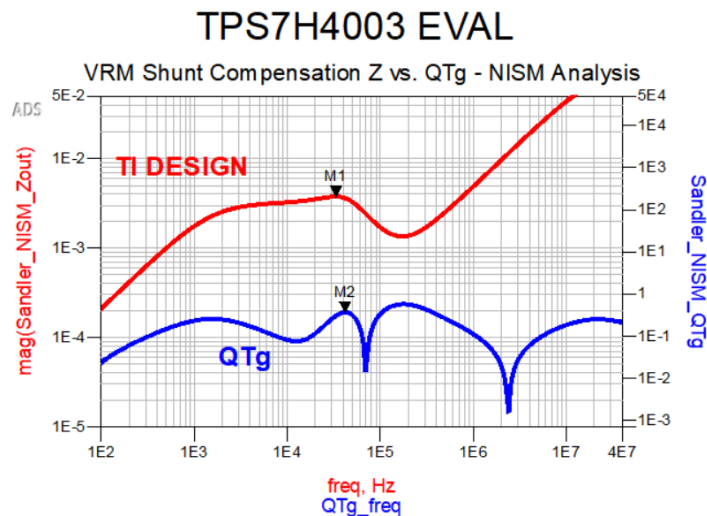NISM* can be used for stability analysis of your VRM State-Space Average Model design with your PDN



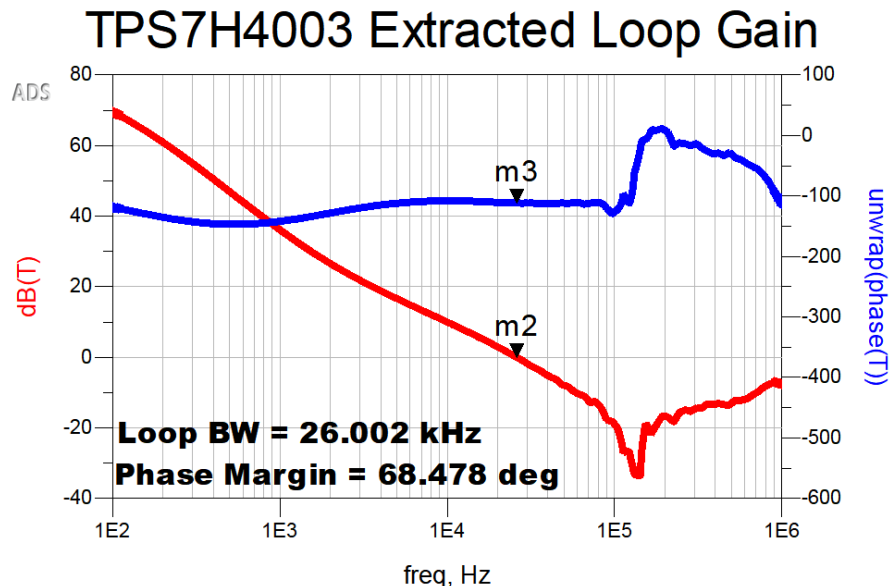Sandler_NISM_PM: >71 degrees
Z Frequency: 33147.205 Hz
Q Frequency: 41734.891 Hz
Effective Q: 0.366




*Picotest Non-Invasive Stability Measurement (NISM)




.... And it works for Multi-Phase and PMICs...

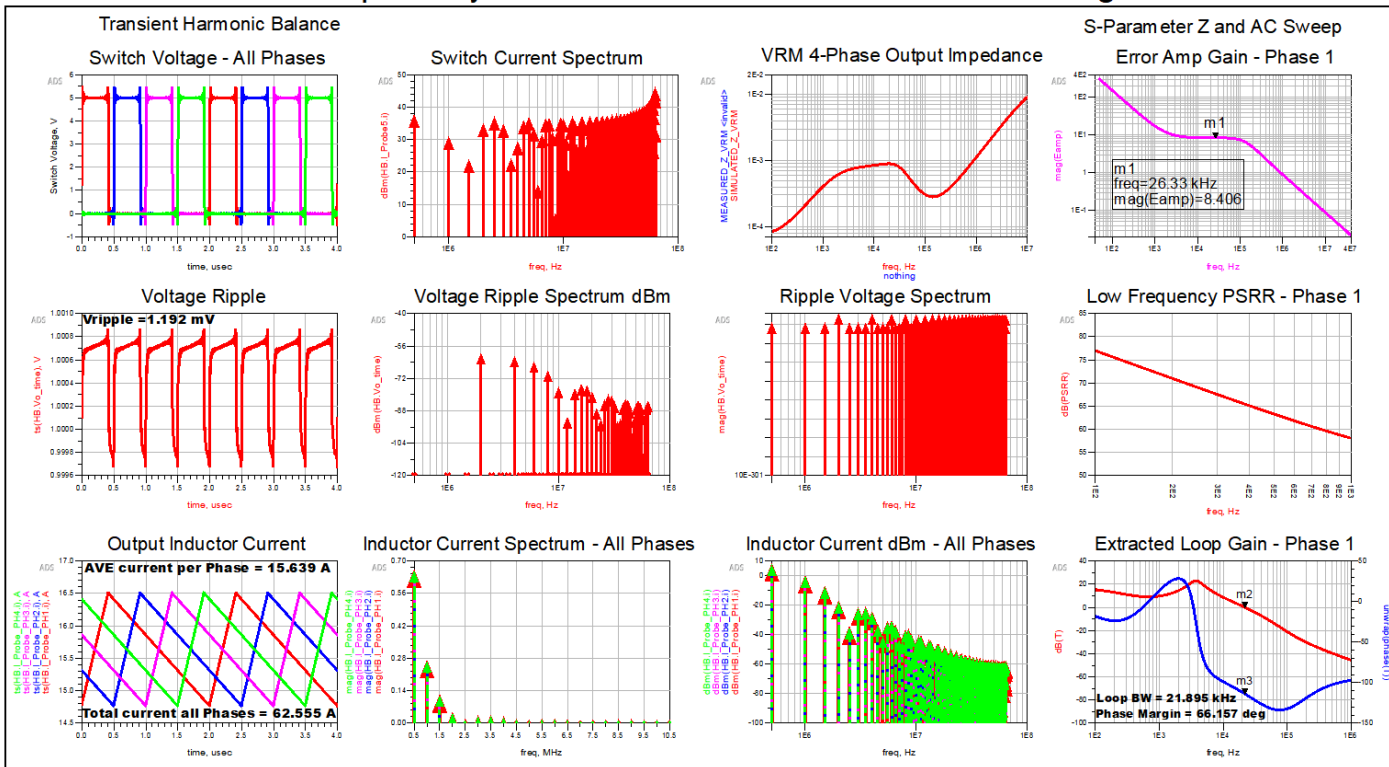State Space Hybrid Model - TPS7H4003 4-PHASE Design



Call to Action

- **Designers need to stop using the L-R, L-R-L-R VRM SPICE models for PI simulations!**
 - The SSAM includes all 5 VRM noise sources for significantly higher fidelity
- **The delineation between Power Integrity and Power Electronics needs to end!**
 - PE designs need to include PCB EM with their VRM designs!
- **Learn to make these simple measurements and try this for yourself**
- **Download the ADS workspace to see the model and simulations**

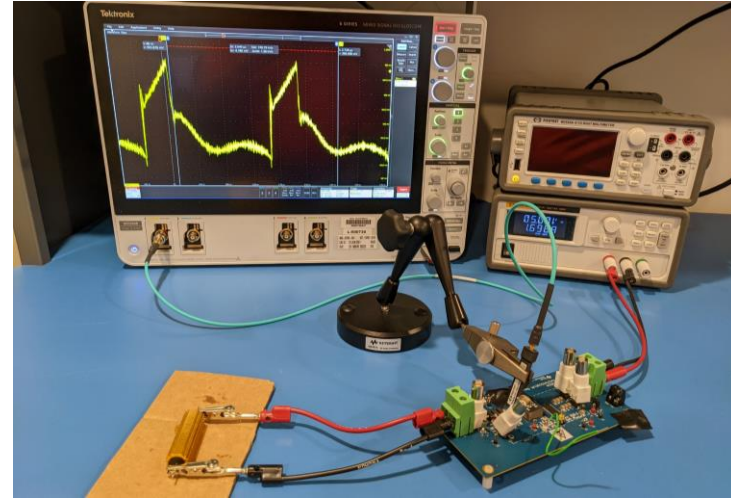

<https://www.picotestonline.com/Designcon2023>

- [How to Design for Power Integrity: Selecting a VRM](#)



Conclusion and Summary

- **Accurate simulation results require a high-fidelity VRM model and the PCB effects!**
- **It takes 4 measurements to build an accurate Sandler State-Space Average VRM model**
 - However, these State-Space Average Models do not need to be perfect!
- **The Sandler State-Space Average VRM Model is.....**
 - Easy to populate for VRMs
 - Supports EM simulations
 - Supports many modes and multi-phase
- **A poor fidelity State-Space Average Model is significantly better than a good R-L VRM model**



Thank you for attending!



QUESTIONS?



References

1. [DesignCon 2017 Slides – Characterizing and Selecting the VRM by Steve Sandler](#)
2. [DesignCon 2017 Paper – Characterizing and Selecting the VRM by Steve Sandler](#)
3. [Bode 100 PSRR Application Note](#)
4. [Techniques for Accurate PSRR Measurements](#)
5. [Measurement Based VRM Modeling](#)
6. [Picotest P2102A-1X 2-port PDN Transmission Line Probe](#)
7. [Application Note - 2-Port Impedance Measurement using the P2102A Probe and Bode 100 VNA](#)
8. [Picotest J2113A Semi-Floating Differential Amplifier](#)
9. [Picotest J2102B Common Mode Transformer](#)
10. [Picotest BNC-BNC 0.25m PDN Cable](#)
11. [Picotest J2120A Line Injector](#)
12. [Bode 100 VNA](#)
13. [TPS7H4003-SEP data sheet, product information and support | TI.com](#)
14. [TPS7H4003EVM Evaluation board | TI.com](#)
15. [TPS7H4003-SEP Radiation-Tolerant 3-V to 7-V Input 18-A Synchronous Buck Converter in Space Enhanced Plastic datasheet](#)
16. [Non-Invasive Stability Measurement](#)
17. S. Sandler, “How to Design for Power Integrity” Keysight sponsored YouTube Video Series: <http://www.keysight.com/find/how-to-videos-for-pi>
18. Keysight PathWave PIPro – <https://www.keysight.com/us/en/product/W3034E/pathwave-pipro.html>

